

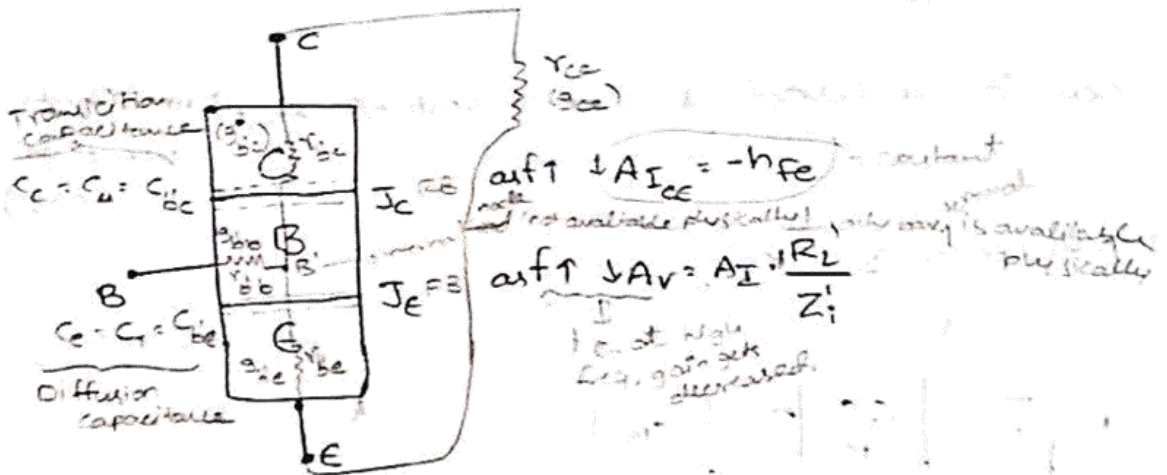


UNIT-3:- HIGH FREQUENCY RESPONSE OF BJT & FET

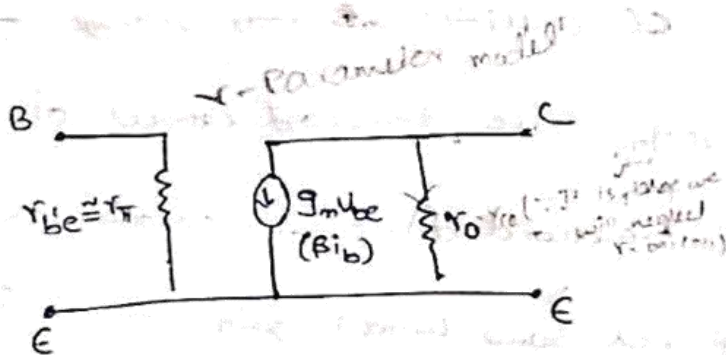- * BJT acts as Amplifier in Active region ($I_C \approx I_E$ & $I_C \approx \beta I_B$)
- * gain of an amplifier falls at LF & HF.
- * gain falls at LF due to coupling (UF) capacitors.
- * gain falls at HF due to internal (or) Junction capacitances (PF capacitances)



BJT high frequency model

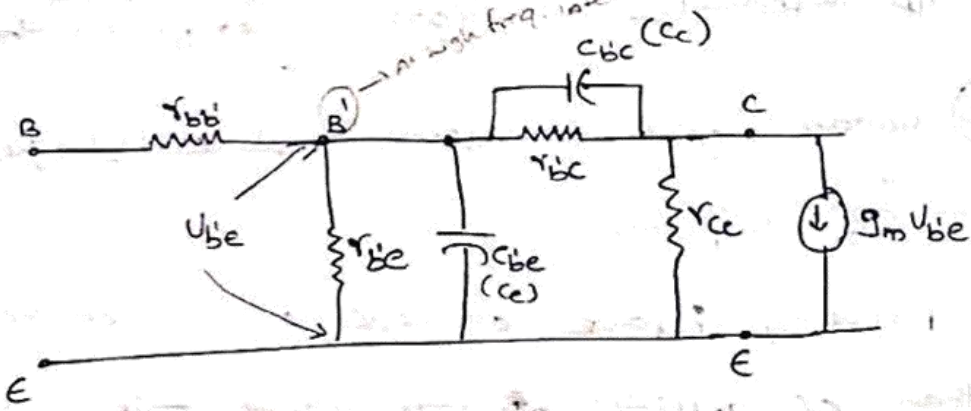

$h_{ie} = r_{\pi} + r_{bb'}$

* All parameters in the high frequency model are assumed to be independent of frequency.

* They may vary with Q-Point i.e., if Q-point is constant all parameters are treated constant for small signal analysis.

* The resistive components of the circuit can be obtained from the low frequency model.

* $r_{bb'}$: Internal ^{node} ~~load~~ in base region which is not physically accessible.

$r_{bb'}$ = Ohmic base spreading resistance b/w External & internal base.

$g_{mV_{be}}$ = Small signal collector current with collector shorted to emitter.

$g_{be} = \frac{1}{r_{be}}$ = Input conductance b/w internal base and emitter.

$g_{bc} = \frac{1}{r_{bc}}$ = feedback conductance b/w internal base & collector.

g_{ce} = o/p conductance b/w collector and emitter.

$C_{be} = C_e = C_{\pi}$ = diffusion capacitance across internal base & emitter.

$C_{bc} = C_c = C_{\mu}$ = Transition (or) Junction capacitance b/w internal base & collector.

→ Typical values of HF BJT Model

(at room temperature & for $I_C = 1.3 \text{ mA}$)

- $g_m = 50 \text{ mA/V}$
- $r_{bc} = 4 \text{ M}\Omega$
- $r_{ce} = 80 \text{ k}\Omega$
- $C_c = 3 \text{ pF}$
- $r_{bb'} = 100 \Omega$
- $C_e = 100 \text{ pF}$
- $r_{be} = r_{\pi} = 1 \text{ k}\Omega$

Important Equations

* $g_m = \text{transconductance}$

$$1) g_m = \frac{I_C}{V_T} = \frac{\beta}{r_{\pi}} = \frac{\alpha}{r_e}$$

$$2) r_{be} = r_{\pi} = \frac{g_m}{\beta} \frac{\beta}{g_m} = \frac{h_{fe}}{g_m}$$

(or)

$$g_{be} = \frac{g_m}{\beta} = \frac{g_m}{h_{fe}}$$

$$3) g_{bc} = h_{re} \cdot g_{be}$$

(or)

$$r_{bc} = h_{re} \cdot r_{be}$$

(or)

$$r_{\pi} = h_{re} \cdot r_{bc}$$

$$4) h_{ie} = r_{bb'} + r_{be}$$

(or)

$$r_{bb'} = h_{ie} - r_{be}$$

$$5) g_{ce} = h_{oe} - g_m h_{re}$$

(or)

$$g_{ce} = h_{oe} - (1 + h_{fe}) g_{bc}$$


$$6) C_c = \frac{\epsilon A}{W} \text{ where } W = \left[\frac{2eV}{q} \left(\frac{1}{N_A} + \frac{1}{N_D} \right) \right]^{1/2}$$

$$7. C_e = \frac{g_m}{2\pi f_T} = g_m \cdot \frac{W_B^2}{2D_B}$$

where $W_B = \text{Base width}$ & $D_B = D_n$ (diffusion constant) for NPN
& $D_B = D_p$ (hole diffusion constant) for PNP.

CE short circuit current gain ($R_L = 0 \Omega$)

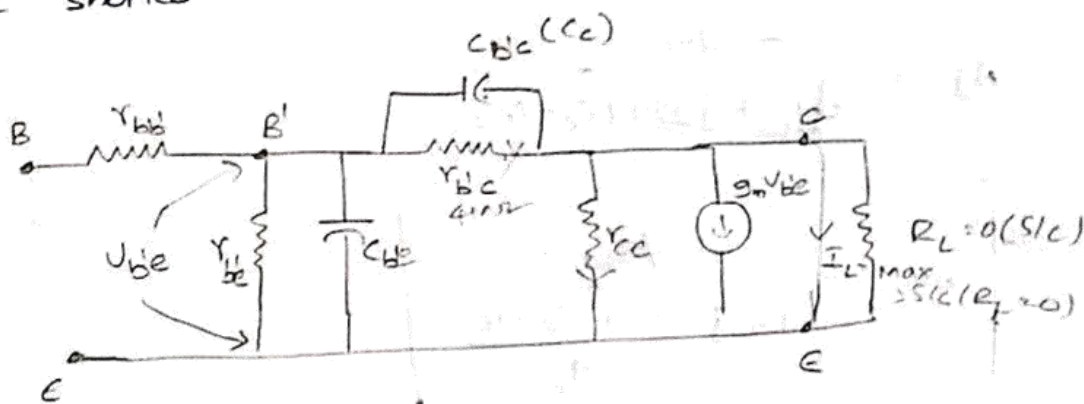Calculation of current gain when collector & Emitter are shorted




1. Effect of r_{cc} is neglected as it is in shunt (||) with $s l c$.

2. Effect of r_{bc} is neglected as it is very high ($4M\Omega$)

r_{bc} = resistance across collector base junction ($4M\Omega$)

($J_c RB$)

↳ more resistance less current

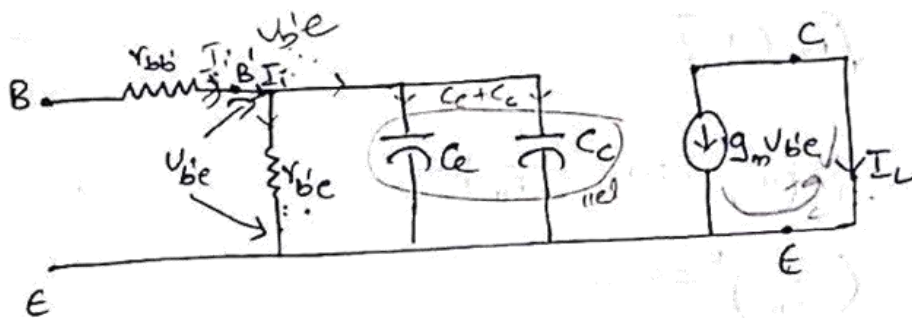

$$\text{Current gain} = A_{I_{R_L=0}} = \frac{I_L}{I_i} \quad \text{--- (1)}$$

$$I_L = -g_m V_{be} \quad \text{--- (2)}$$

(o/p direction)

$$\frac{V_{be}}{I_i} = \frac{V_{be}}{r_{be}} + \frac{V_{be}}{X_{C_e+C_c}} = V_{be} \left[\frac{1}{r_{be}} + \frac{1}{j 2\pi f (C_e + C_c)} \right]$$

$$I_i = V_{be} [g_m + j 2\pi f (C_e + C_c)] \quad \text{--- (3)}$$

now

$$A_I = \frac{I_L}{I_i} = \frac{-g_m v_{be}}{v_{be} [g_{be} + j2\pi f (C_c + C_e)]}$$

$$A_I = \frac{-g_m}{g_{be} + j2\pi f (C_c + C_e)}$$

$$A_I = \frac{(-g_m/g_{be})}{1 + j \frac{2\pi f (C_c + C_e)}{g_{be}}}$$

formula ②

$$g_{be} = \frac{g_m}{\beta} = \frac{g_m}{h_{fe}}$$

$$A_I = \frac{-h_{fe}}{1 + j \frac{2\pi f (C_c + C_e)}{g_{be}}} \cdot f \rightarrow \text{input signal freq.}$$

$$A_I = \frac{-h_{fe}}{1 + j \left(\frac{f}{f_H}\right)} \quad \text{where } f_H = \frac{g_{be}}{2\pi (C_c + C_e)} = \text{constant}$$

f_H = upper cut off frequency

f = input signal frequency

$$|A_I| = \frac{h_{fe}}{\sqrt{1 + \left(\frac{f}{f_H}\right)^2}}$$


* (a) if $f < f_H$ then $\left(\frac{f}{f_H}\right) < 1$

$$\left(\frac{f}{f_H}\right)^2 \ll 1$$

$$\text{SO } |A_I| \approx h_{fe}$$

* (b) if $f > f_H$ then $\left(\frac{f}{f_H}\right) > 1$ & $\left(\frac{f}{f_H}\right)^2 \gg 1$

$$\text{SO } |A_I| = \frac{h_{fe}}{\left(\frac{f}{f_H}\right)} = \frac{f_H \cdot h_{fe}}{f} = \text{gain } \downarrow \text{ as } f > f_H$$

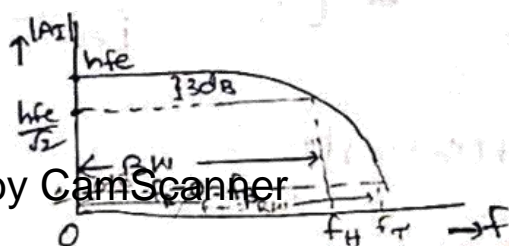

f_H when collector & emitter are shorted, it is defined as f_B = Bandwidth of CE when C & E are shorted.

f_T = Unity gain cut-off frequency

f_T = unity gain BW product.

f_T = It is the frequency at which CE S/C A_I reaches (or) reduces to unity.

$$|A_I| = \frac{h_{fe}}{\sqrt{1 + \left(\frac{f}{f_B}\right)^2}}$$

$$\therefore f > f_B, \left(\frac{f}{f_B}\right)^2 \gg 1$$

$$|A_I| \approx \frac{h_{fe}}{\left(\frac{f}{f_B}\right)}$$

K.K.T at $f = f_T$ then $A_I = 1$

$$1 = \frac{h_{fe}}{\left(\frac{f_T}{f_B}\right)} \Rightarrow \boxed{f_T = h_{fe} \cdot f_B}$$




$$\boxed{f_T = h_{fe} \cdot f_B} \quad \left| \quad \boxed{f_T = \text{gain} \times \text{BW}} \right.$$

product's constant


low freq. \times BW of CE amp
Current gain with $R_L \approx 0 \Omega$

if current gain = 1 $\Rightarrow f_T = \text{BW at } A_I = 1$

BJT high frequency response

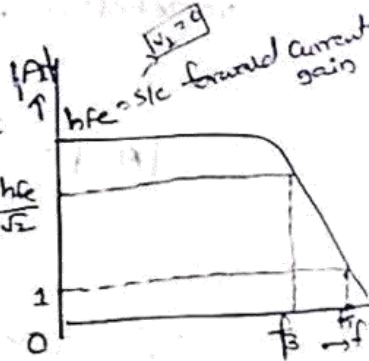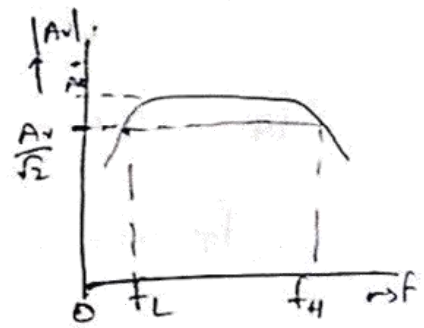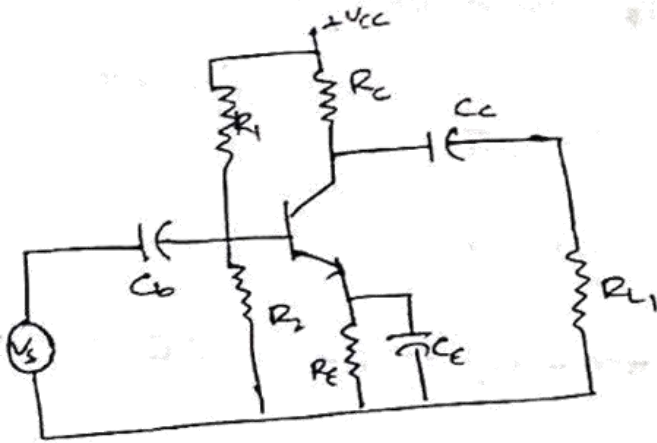

RL into effect

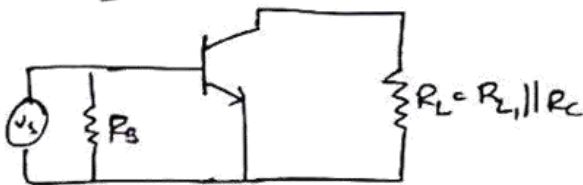

$$A_I = \frac{-h_{fe}}{1 + j(f/f_H)}$$

$$|A_I| = \frac{h_{fe}}{\sqrt{1 + (f/f_H)^2}}$$

f_B = BW of CE amplifier with s/c gp


f_B = f_T - Cutt of frequency

$$f_T = \frac{g_{mbe}}{2\pi(C_c + C_e)} = \frac{1}{2\pi r_{be}(C_c + C_e)}$$


$$f_T = h_{fe} \cdot f_B = \text{gain} \times \text{BW}$$

$$= \text{gain} \times \text{BW product}$$

f_T = unity gain BW (i.e. gain = 1)


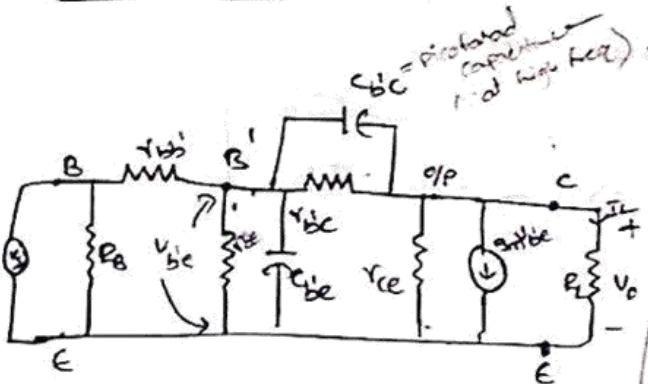


using miller's theorem,

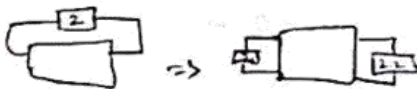

$$Z_1 = \frac{Z}{1 - A_{V1}} = \frac{1/j\omega C}{1 - A_{V1}} = \frac{1}{j\omega C(1 - A_{V1})}$$
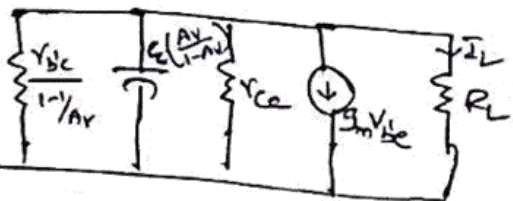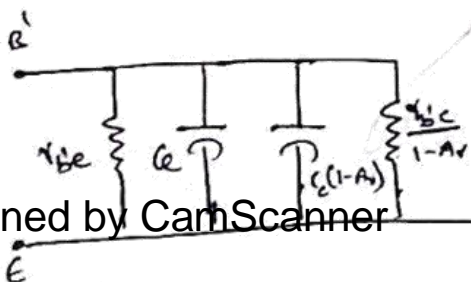
$$Z_2 = \frac{Z}{1 - A_{V2}} \text{ where } A_{V1} = \text{MF voltage gain}$$




$A_v = \text{voltage gain at MF} = \frac{V_o}{V_{be}} = \frac{V_{ce}}{V_{be}}$

at MF, all PF capacitances (C_c, C_e) act as o/c

$V_o = -g_m V_{be} R_L$

$\frac{V_o}{V_{be}} = A_v = -g_m R_L$

$A_v = -100$

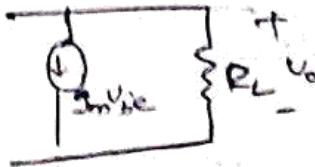

Input side

1. $\frac{Y_{b'e}}{1 - A_v} = \frac{4M\Omega}{1 - (-100)} = \frac{4M\Omega}{101} \approx 40K\Omega$

$\frac{Y_{b'c}}{1 - A_v}$ can be neglected as it is in ||el with $Y_{b'e}$ ($\approx 1K\Omega$)

Output side


1. $\frac{Y_{b'c}}{1 - Y_{av}} \approx Y_{b'c} = 4M\Omega$

This can be neglected as it is in ||el with R_L ($\approx 2K\Omega$)

2. $Y_{ce} = 80K\Omega (>> R_L)$

Y_{ce} can be neglected as it is in ||el with R_L ($\approx 2K\Omega$)

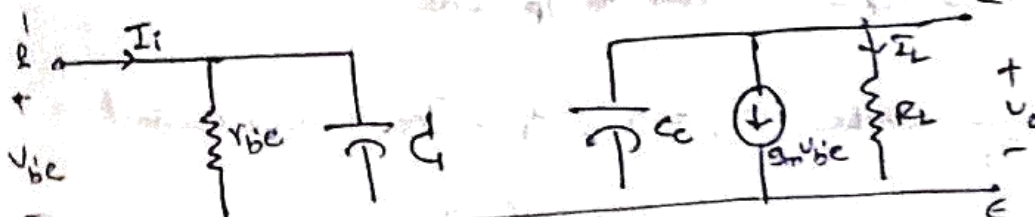3. $C_c \left(\frac{A_v}{A_v - 1} \right) \approx C_c$




where $C_c = C_e + C_c (1 - A_v)$

$$I_L = -g_m V_{be} \times \frac{\frac{1}{j\omega C_c}}{\frac{1}{j\omega C_c} + R_L}$$


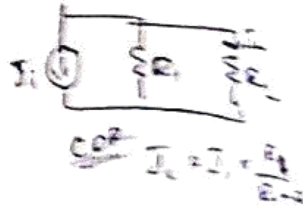
$$I_L = \frac{-g_m V_{be}}{1 + j\omega R_L C_c} = \frac{-g_m V_{be}}{1 + j2\pi f R_L C_c}$$



$$I_L = \frac{-g_m V_{be}}{1 + j\left(\frac{f}{f_{H_0}}\right)}$$

where $f_{H_0} = \frac{1}{2\pi R_L C_c}$ — (1)

$f_{H_0} = \frac{1}{2\pi T_0} =$ upper cut off freq. due to op.

where $T_0 = R_L C_c =$ op time constant

$$I_i = \frac{V_{be}}{r_{be}} + \frac{V_{be}}{\frac{1}{j\omega C_c}} = V_{be} \left[\frac{1}{r_{be}} + j\omega C_c \right]$$

$$I_i = V_{be} \left[\frac{1 + j\omega r_{be} C_c}{r_{be}} \right] \quad \text{--- (2)}$$


$$A_{I \text{ with } R_L} = \frac{I_L}{I_i}$$

$$A_{I \text{ with } R_L} = \frac{-g_m r_{be}}{(1 + jf/f_{H_0})(1 + j\omega r_{be} C_c)}$$

$$\frac{-g_m r_{be}}{(1 + jf/f_{H_0})(1 + jf/f_{H_i})}$$

where $f_{H_i} = \frac{1}{2\pi r_{be} C_c} =$ upper cut off freq. due to i/p side

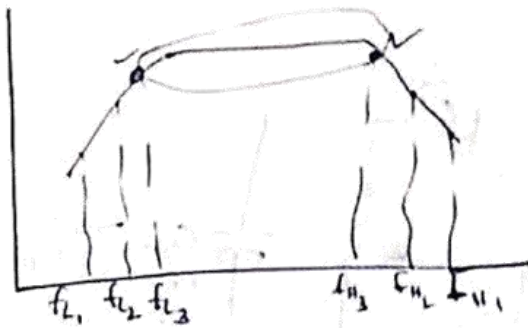$f_{H_i} = \frac{1}{2\pi T_i}$ where $T_i = r_{be} C_c =$ Input time constant



$f_L = \text{highest } (f_{L1}, f_{L2}, f_{L3})$

$f_H = \text{lowest } (f_{H1}, f_{H2}, f_{H3})$

$$\tau_i = r_{be} \cdot C_i = r_{be} [C_e + C_c (1 - A_v)]$$

$$\tau_i = 1k\Omega [100pF + 3pF (1 + 100)]$$

$$\tau_i = 403 \text{ nsec}$$

$$\tau_o = R_L \cdot C_c = 2k\Omega \times 3pF$$

$$\tau_o = 6 \text{ nsec}$$


Since $\tau_o < \tau_i$ so $f_{H1} < f_{H0}$

$$\text{Hence } f_{H \text{ overall}} = f_{H1} = \frac{1}{2\pi r_{be} \cdot C_i}$$

Disadvantage overall $f_H = f_{H1}$ is constant for given CE amplifier which can't be modified once the amplifier ckt is designed.

to avoid this disadvantage, we go for Remedy.

Remedy

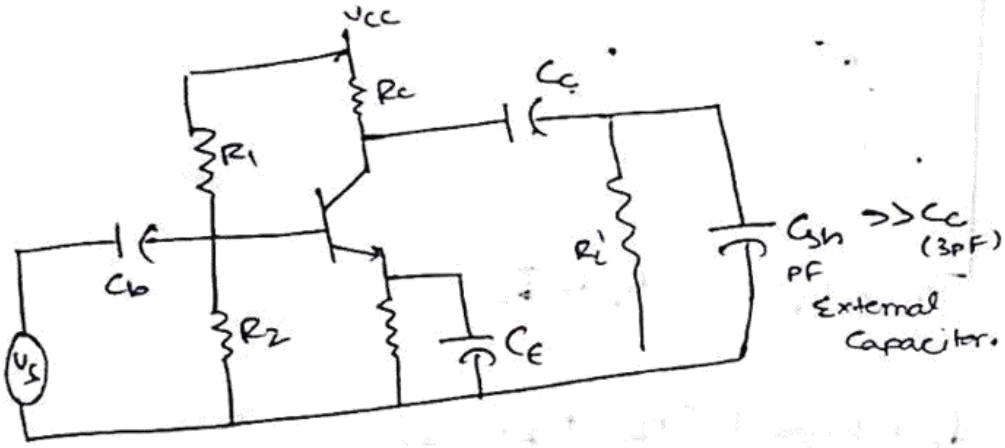


$$f_{H_i} = \frac{1}{2\pi Y_{bc} C_b} \quad \text{and} \quad f_{H_o} = \frac{1}{2\pi R_L C_{sh}}$$

$$f_{H_o} < f_{H_i}$$

So $f_H \approx f_{H_o}$ overall

choose C_{sh} such that

$$\tau_o > \tau_i$$

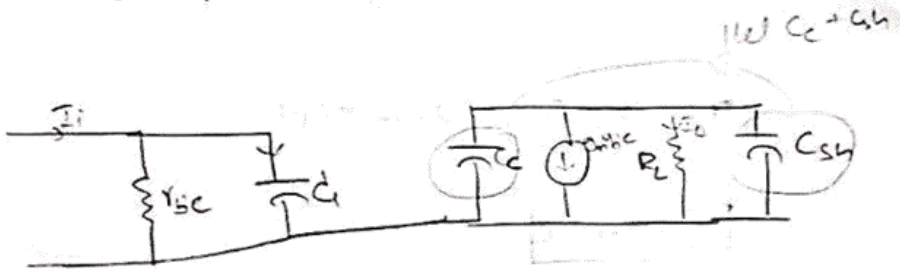

Problem

The h-parameters of a CE-Amplifier $h_{ie} = 600\Omega$, $h_{fe} = 100$, $h_{re} = 10^{-4}$, $h_{oe} = 4 \times 10^{-3} S$. If $C_c = 3pF$, $I_C = 5mA$ and $A_V = 10$ at $10MHz$. find f_B , f_T , r_{bc} , r_{bb} , C_e .

$$r_{bc} = \frac{h_{re}}{h_{fe}} = \frac{B}{g_m}$$

$$g_m = \frac{I_C}{V_T} = \frac{5mA}{26mV} = \frac{5}{26}$$

$$r_{bc} = \frac{h_{re}}{g_m} = \frac{100 \times 26}{5} = 520\Omega$$

$$A_V = \frac{-h_{fe}}{1 + jf/f_B}$$

$$|A_V| = \frac{h_{fe}}{\sqrt{1 + (f/f_B)^2}}$$

Given $|A_V| = 10$ at $f = 10MHz$

$$f_B = 10^6 Hz$$

$$f_T = \beta f_B = h_{fe} \cdot f_B = 10^8 Hz$$

$$r_{bb'} = h_{ie} - r_{be}$$

$$= 600 - 520$$

$$= 80 \Omega$$

$$f_T = \frac{g_m}{2\pi(C_c + C_e)}$$

$$10^8 \text{ Hz} = \frac{5}{26(3.14)(23 \times 10^{-12} + C_e)}$$

$$3 \times 10^{-12} + C_e = \frac{5 \times 10^{-8}}{26(3.14) \times 10^2}$$

$$= \frac{6.12 \times 10^{-10}}{2}$$

$$C_e = \frac{6.07 \times 10^{-10}}{2}$$

$$C_e = \frac{6.07}{2} \text{ PF}$$

p) SIC, C_e, A_I of a transistor is 25 at a freq of 2 MHz. if $f_B = 20 \text{ kHz}$. Calc h_{fe}, f_T & A_I at 10 MHz

Sol $|A_I| = 25$ at $f = 2 \text{ MHz}$

$$f_B = 20 \text{ kHz}$$

$$|A_I| = \frac{h_{fe}}{\sqrt{1 + (f/f_B)^2}}$$

$$25 = \frac{h_{fe}}{\sqrt{1 + \left(\frac{2 \times 10^6}{20 \times 10^3}\right)^2}}$$

$$h_{fe} = 25 \times 2$$

$$f_T = \beta f_B$$

$$= 25 \times (20) \times 10^3$$

$$= 500 \times 10^3$$


$$f_T = 500 \text{ kHz}$$

at $f = 10 \text{ MHz}$

$$|A_I| = \frac{h_{fe}}{\sqrt{1 + (f/f_B)^2}}$$


$$= \frac{251}{\sqrt{1 + \left(\frac{10 \text{ M}}{200 \text{ K}}\right)^2}} = 5.023$$

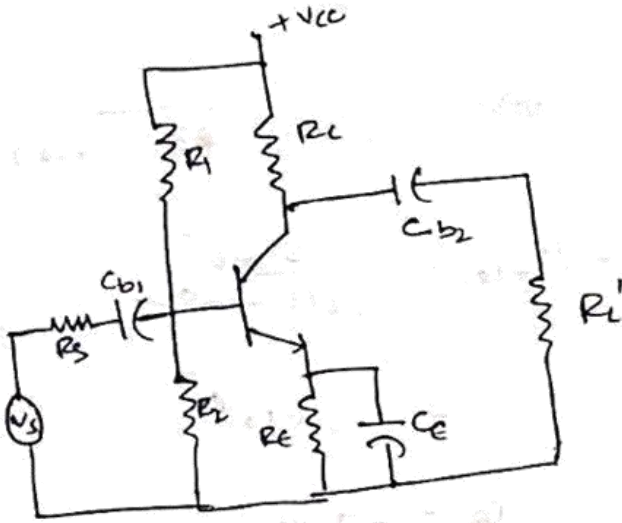CE Amplifier at HF with practical voltage source
 (V_s with R_s & R_L)



At high f , C_{bc} & C_{ce} current gain reduces at low f of constant

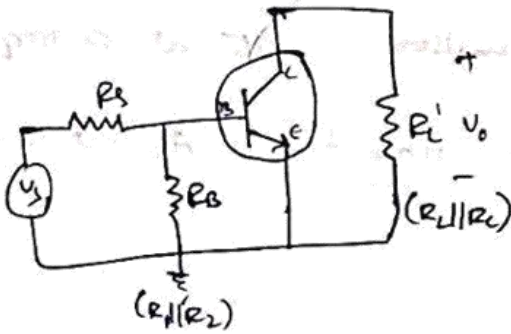→ Replaced with high freq equivalent model.




(i) C_E with $R_L = 0$ (V_s with R_s)


(ii) CE Amp with $R_L \neq 0$ (V_s with R_s)

(iii) CE Amp with $R_L \neq 0$ (V_s with $R_s \neq 0$)

→ Voltage gain, A_V
 → f_H

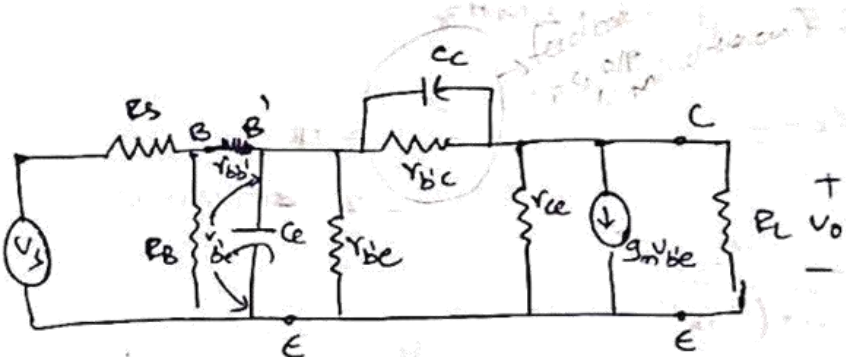


Using Miller Theorem

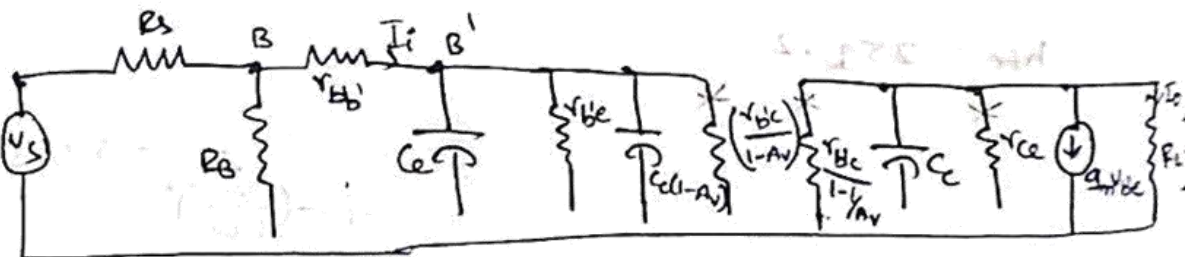

$A_v = \text{Mid frequency voltage gain}$

$$A_v = -g_m R_L \gg 1$$

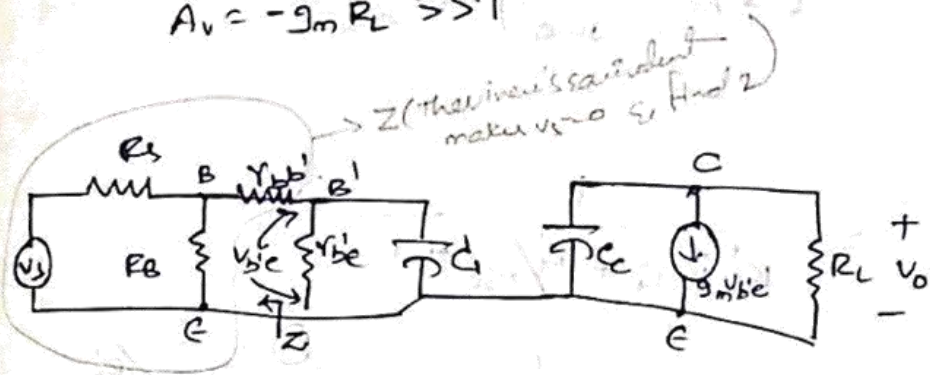

where $C = C_E + C_C(1 + g_m R_L)$

$$V_o = -g_m V_{be} \left[R_L \parallel \frac{1}{j\omega C} \right]$$



$$= -g_m V_{be} \left[\frac{R_L \cdot \frac{1}{j\omega C}}{R_L + \frac{1}{j\omega C}} \right]$$

$$V_o = \frac{-g_m R_L V_{be}}{1 + j\omega R_L C}$$

$$\frac{V_o}{V_{be}} = \frac{-g_m R_L}{1 + j \left(\frac{f}{f_{H0}} \right)}$$

where $f_{H0} = \frac{1}{2\pi R_L C}$ upper cut off frequency due to op node.
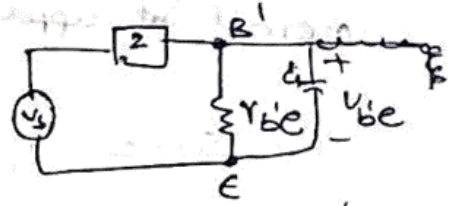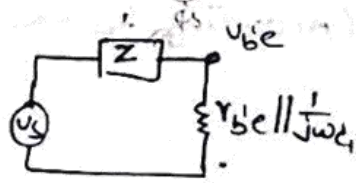
$$A_v = \frac{V_o}{V_s} = \frac{V_o}{V_{be}} \times \frac{V_{be}}{V_s}$$



where $Z = R_s \parallel (R_B + r_{bb'})$

$V_{DR} \equiv V = V_s \times \frac{\text{that resistance}}{\text{Sum of resistance}}$

$$V_{DR} \approx \frac{R_s + r_{bb'}}{R_s + r_{bb'}} = R_s'$$

$$V_{be} = \frac{[r_{be} \parallel \frac{1}{j\omega C}]}{R_s' + r_{be} \parallel \frac{1}{j\omega C}} V_s$$

$$\frac{V_{be}}{V_s} = \frac{r_{be} \left(\frac{1}{j\omega C} \right)}{R_s' \left(r_{be} + \frac{1}{j\omega C} \right) + r_{be} \left(\frac{1}{j\omega C} \right)}$$

$$\frac{V_{be}}{V_s} = \frac{(r_{be} / j\omega C_c)}{[R_s' r_{be} + \frac{R_s'}{j\omega C_c}] + (\frac{r_{be}}{j\omega C_c})}$$

$$= \frac{1}{R_s' j\omega C_c + R_s' / r_{be} + 1}$$

$$= \frac{1}{R_s' (j\omega C_c + g_{be}) + 1} \approx \frac{1/R_s'}{(j\omega C_c + g_{be}) + 1/R_s'}$$

$$= \frac{G_s'}{j\omega C_c + g_{be} + G_s'}$$

$$A_v = \frac{V_o}{V_{be}} \times \frac{V_{be}}{V_s} = \left(\frac{-g_m R_c}{1 + j(f/f_{Lb})} \right) \cdot \left(\frac{G_s'}{j\omega C_c + g_{be} + G_s'} \right)$$

$$f_{Hi} = \frac{1}{2\pi R_i C_i} = \text{upper cut off frequency due to i/p node.}$$

$$f_{Hi} = \frac{1}{2\pi T_i}$$

then $R_i = R_s' \parallel r_{be}$

$$C_i = C_c = C_e + C_c (1 + g_m R_c)$$

overall of upper cutoff frequency = $f_H = \min(f_{Hi}, f_{Ho})$

Since $T_i \gg T_o$ (According to standard value)

$$f_{Hi} < f_{Ho}$$



Hence $f_H = f_{Hi} = \frac{1}{2\pi R_i C_i}$

Disadv $f_{Hi} = \text{constant}$

→ Emitter follower (common collector) at HF

→ A_v of CC & f_H of CC

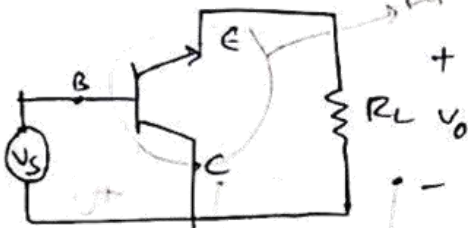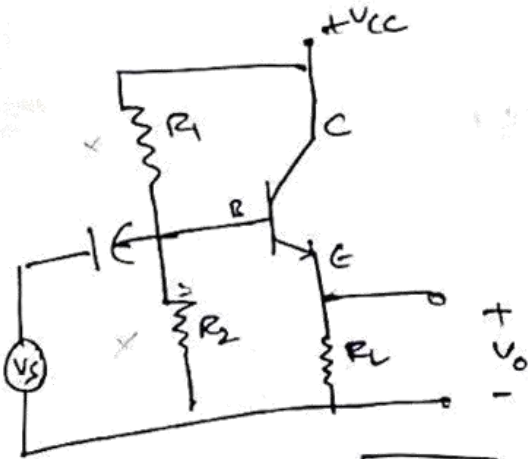
* $A_{v_m} \approx 1$ (unity voltage gain) for CC



Replacing with equivalent HF model:

R_E is not considered because its value is high


E' is internal base node

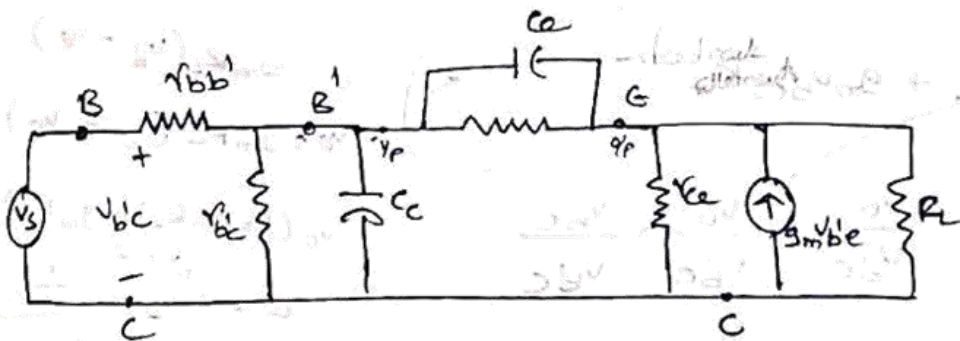

Significant direction is always from collector to emitter

$$A_v = \frac{V_o}{V_{i'c}}$$

Use Miller's theorem

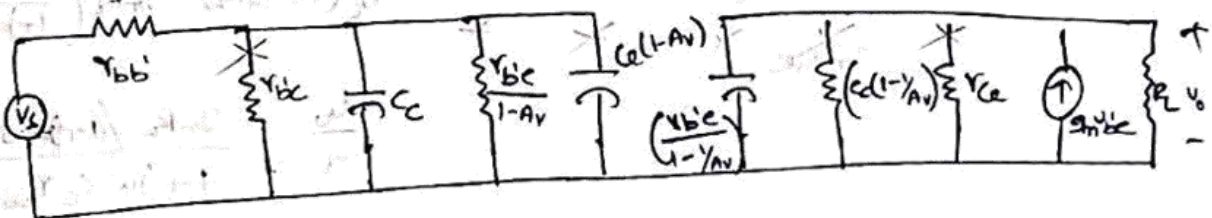

At MF, CC $A_v = 1$

1/p side

1) $r_{be} = \alpha (r_{i'c})$

2) $C_e (1 - A_v)$

= 0

$X_{Ce} = \frac{1}{j\omega C_e} = \frac{1}{0} = \infty (ole)$

o/p side

$$1) \frac{r_{b'e}}{1 - 1/A_v} \approx \infty \text{ (o/c)}$$


$$2) C_e(1 - 1/A_v) \approx 0$$

$$X_{C_e} = \frac{1}{j\omega C_e} \approx \frac{1}{0} \approx \infty \text{ (o/c)}$$

$$3) r_{C_e} = 80k\Omega \gg R_L$$

r_{C_e} can be removed

Equivalent circuit

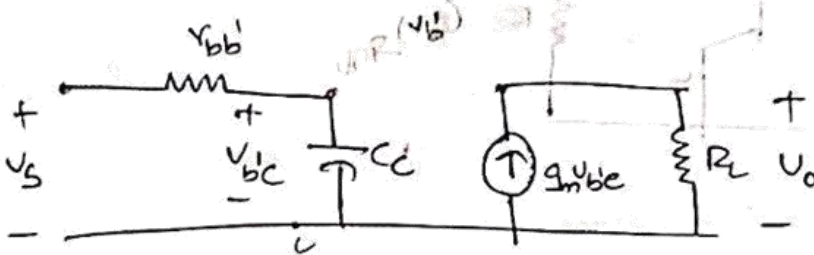

$$v_o = + g_m v_{b'e} R_L \Rightarrow v_o = g_m R_L (v_b' - v_e)$$

$$v_o = g_m R_L (v_b' - v_o)$$

$$v_o (1 + g_m R_L) = g_m R_L v_b'$$

where $v_b' = \frac{1}{j\omega C_e} \times v_s$
 $\frac{1}{r_{bb'} + \frac{1}{j\omega C_e}}$

$$\Rightarrow v_b' = \frac{v_s}{1 + j\omega C_e r_{bb'}}$$

$$A_v = \frac{v_o}{v_{b'e}} = \frac{v_o}{v_b'} \times \frac{v_b'}{v_{b'e}}$$

$$\times f_H = \frac{1}{2\pi r_{bb'} C_e} \approx \text{upper cut off frequency}$$

get ratio of $\frac{v_{b'e}}{v_b'}$ by using KCL at b' node.

$$v_o (1 + g_m R_L) = g_m R_L \left(\frac{1}{1 + j\omega C_e r_{bb'}} \right) v_s$$

$$\frac{v_o}{v_s} = \frac{g_m R_L / (1 + g_m R_L)}{1 + j\omega C_e r_{bb'}}$$

$$A_v = \frac{v_o}{v_s} = \frac{(g_m R_L / (1 + g_m R_L))}{1 + j(f/f_H)}$$

where



$$f_H = \frac{1}{2\pi r_{bb'} C_e}$$

since $g_m R_L \gg 1$

$$A_v \approx \frac{1}{1 + j(f/f_H)}$$


for $f > f_H$ $A_v < 1$

* Problem:- CC amp with C_L

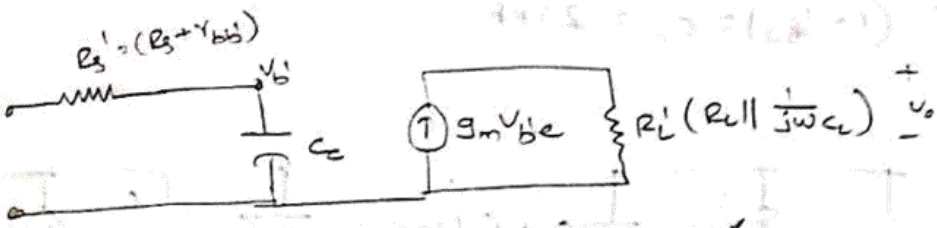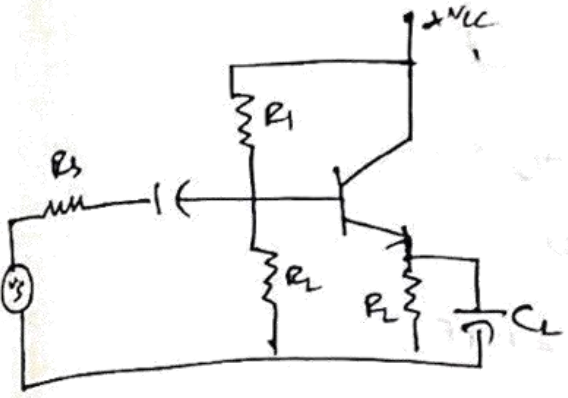

$$V_o = g_m R_L' (V_{b'} - V_e)$$

P1)

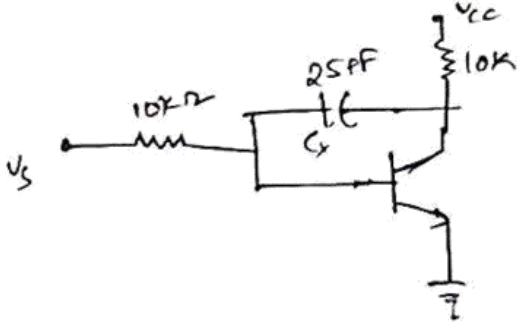


middle theorem

find f_H if $g_m = 5mA/V$

$r_{\pi} = 20k\Omega$
 r_{be}

$C_{\pi} = 1.5PF$


$C_u = 0.5PF$

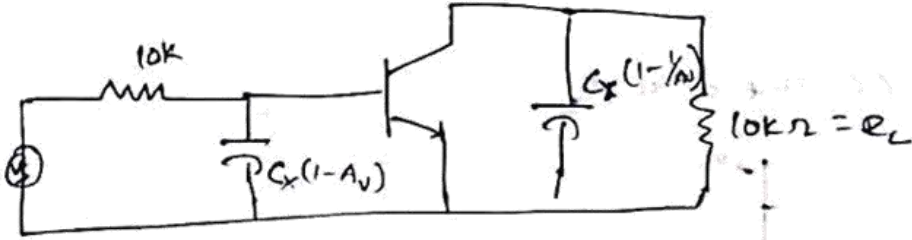

where $A_v = -g_m R_L = -5mA/V \times 10k$
 $= -50$

$C_x(1-A_v) = 25 \times 51 = 1275PF$

$C_x(1-1/50) \approx C_x = 25PF$

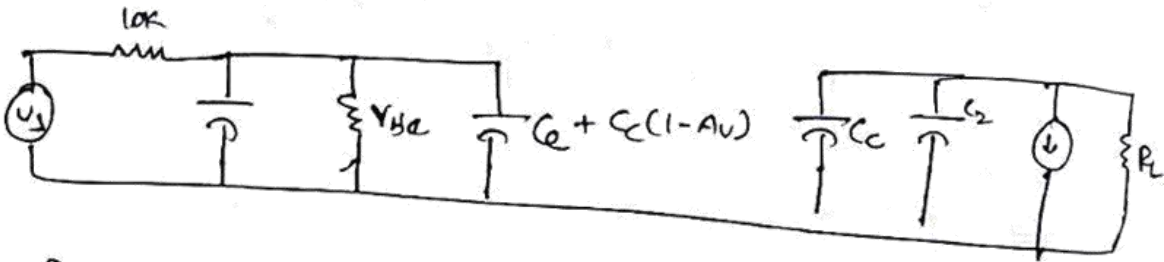

$f_{Hi} = \frac{1}{2\pi \tau_i}$

where $\tau_i = R_i C_i$

where $R_i = 10 || r_{be}$

$= 10 || 20$

$C_i = C_1 + C_2 + C_u(1-A_v)$

$= 1275 + 1.5 + 0.5(51)$

$f_{Ho} = \frac{1}{2\pi \tau_o}$

$\tau_o = R_o C_o$

where

$R_o = R_L = 10k\Omega$

$C_o = C_c + C_u$

$= 0.5 + 25$

$\tau_i \gg \tau_o$ so $f_H \approx f_i$

An NPN Transistor with $C_{\pi} = 0.3 \text{ pF}$ & unity gain cut off

freq. $f_T = 400 \text{ MHz}$ at a DC bias current of $I_C = 1 \text{ mA}$.

find $C_C = ?$ $C_{\mu} = ?$

$$f_T = \frac{g_m}{2\pi(C_c + C_{\mu})} = \frac{g_m}{2\pi(C_{\pi} + C_{\mu})} = \frac{1}{26 \times 2\pi(0.3 \text{ pF} + C_{\mu})}$$

where $g_m = \frac{I_C}{V_T} = \frac{1 \text{ mA}}{26 \text{ mV}} = \frac{1}{26} \times 10^{-3} \text{ A/V}$

$$C_{\mu} = 1.53 \times 10^{-11} - 0.3 \times 10^{-12}$$


$$C_{\mu} = 1.5 \times 10^{-11} \text{ F}$$

→ for a NPN BJT $g_m = 38 \text{ mA/V}$ & $C_{\mu} = 10^{-14} \text{ F}$ $C_{\pi} = 4 \times 10^{-13} \text{ F}$

$\beta = h_{fe} = 90$ find f_T & f_{β}

$$f_T = \frac{g_m}{2\pi(C_c + C_{\mu})} = \frac{38 \times 10^3}{2 \times 3.14(10^{-14} + 4 \times 10^{-13})}$$

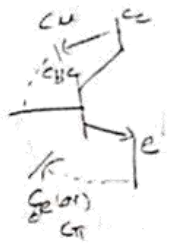C_{μ} & C_{π} are internal (pF) capacitances exists at high freq.



$$f_T = 1.47 \times 10^{10}$$

$$f_T = h_{fe} f_{\beta}$$

$$\frac{1.47 \times 10^{10}}{90} = f_{\beta}$$

$$f_{\beta} = 1.63 \times 10^8$$

