

IV. FEEDBACK AMPLIFIERS

Types of Basic Amplifiers and their Local characteristics:

Generally, Amplifiers without feedback are referred as basic amplifiers.

we know the characteristics of Amplifiers as Gain, Band width, input and output impedances etc....

* Basic Amplifiers have been classified into four broad categories.

The relative magnitude of o/p impedance as compared to the source impedance, and that of output impedance as compared to load impedance are the factors which determine the category of the amplifier.

1. Voltage Amplifiers



2. Current Amplifiers

3. Transconductance Amplifiers

4. Transresistance Amplifiers

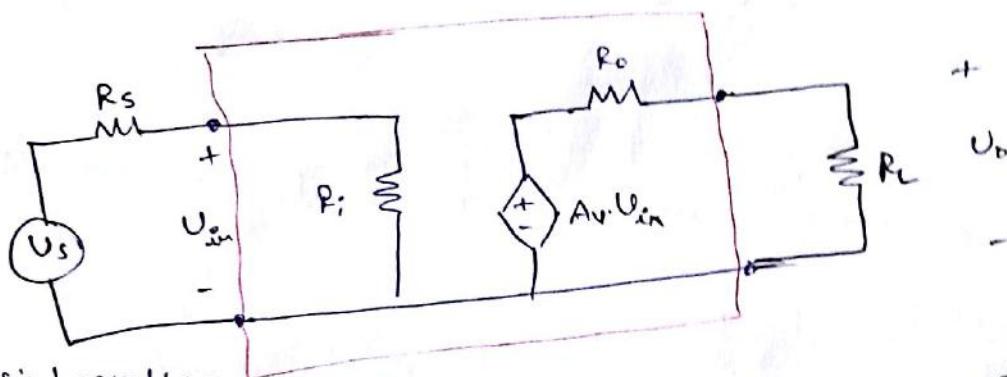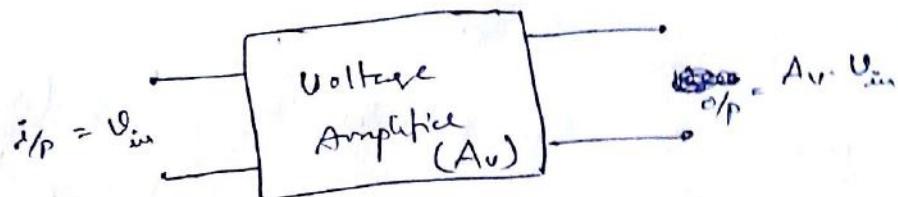1. Voltage Amplifier:

which takes voltage as input signal and produces ~~op~~ output as voltage signal.



U_i = original i/p signal applied to amp

U_{in} = effective i/p signal across i/p load R_s

$Av \cdot U_{in}$ = o/p voltage generated Fig. equivalent circuit of voltage amplifier.

U_o = o/p voltage fed to load R_L

$$U_{in} = \frac{R_i}{R_i + R_s} \times U_s \quad \text{and} \quad U_o = \frac{R_L}{R_L + R_o} \times Av \cdot U_{in}$$

if $R_o \gg R_s$ then $U_{in} \approx U_s$

$$\therefore U_o = \frac{R_L}{R_L + R_o} \times Av \cdot U_s$$

~~Op~~ ~~Output~~

and if $R_o \ll R_L$ then

$$U_o \approx Av \cdot U_s$$

→ Characteristics of Voltage Amps:

* Ideal characteristics of Voltage Amps.

$$1. Av = \infty$$

2. Av must be stable

$$3. BW = \infty$$

$$4. R_i = \infty$$



$$5. R_o = 0$$

* Ideal Voltage Amp has infinite i/p resistance & zero o/p resistance



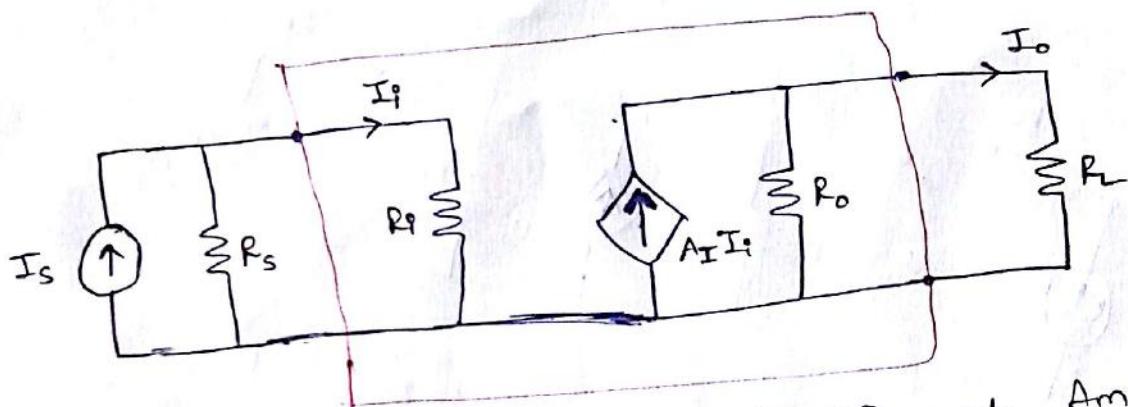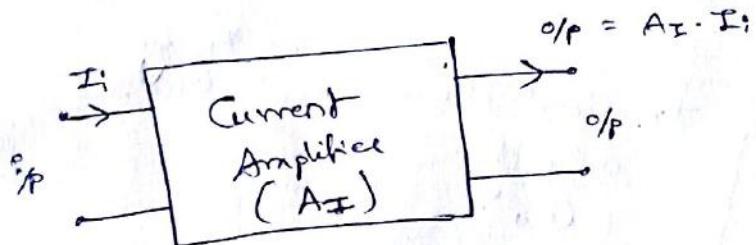2. Current Amplifier:

which accepts current as input signal and produces output signal as current



Figs: Equivalent circuit of Current Amplifier.

Using current division rule,

$$I_o = \frac{R_s}{R_s + R_i} \times I_s \quad \text{and}$$

$$I_o = \frac{R_o}{R_o + R_L} \times A_I \cdot I_s$$

if $R_i \ll R_s$ then $I_o \approx I_s$

$$\text{So } I_o = \frac{R_o}{R_o + R_L} \times A_I \cdot I_s$$

$$I_o \approx A_I \cdot I_s$$

and if $R_o \gg R_L$ then

* Ideal characteristics of Current Amplifier are:

$$1. A_I = \infty$$

$$4. R_i = 0$$

2. ~~A_I~~ must be stable

$$5. R_o = \infty$$

$$3. BW = \infty$$

* Ideal Current Amp has zero i/p resistance & infinite o/p resistance

3. Transconductance Amplifiers: $G_m = \frac{I_o}{V_{in}}$

It accepts voltage as input signal
and provides current as output signal.

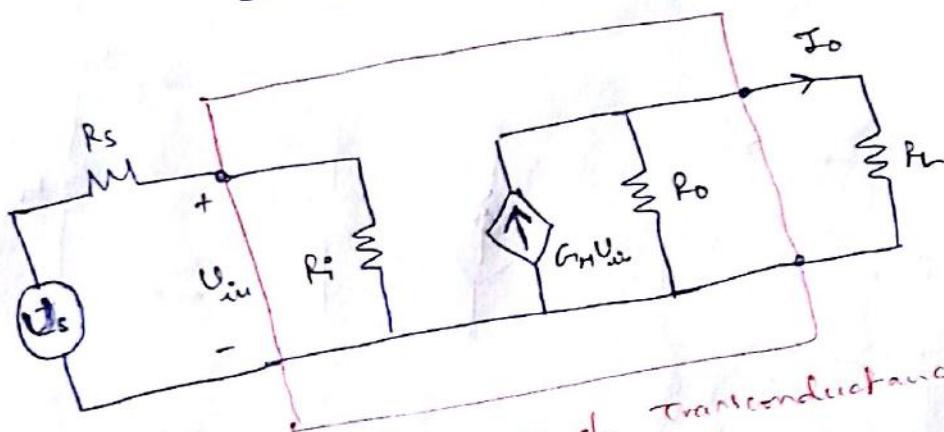
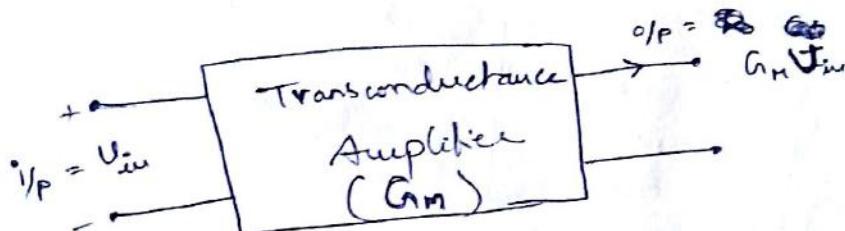


Fig: Equivalent circuit of Transconductance Amp

$$V_{in} = \frac{R_i}{R_i + R_s} \times V_s \quad \text{and} \quad I_o = \frac{R_o}{R_o + R_L} \times G_m V_{in}$$

if $R_i \gg R_s$ and $R_o \gg R_L$ then $I_o \approx G_m V_s$

* Characteristics of Transconductance Amp:

1. Very high & stable Transconductance gain (G_m)

1. Very high & stable Transconductance gain (G_m)
2. Very high BW
3. Very high i/p & o/p impedances.

* Ideal characteristics of Transconductance Amp:

1. $G_m = \infty$

2. G_m must be stable

3. $BW = \infty$



4. $R_i = \infty$

5. $R_o = \infty$

* Ideal Transconductance Amp has infinite input and infinite output impedances.

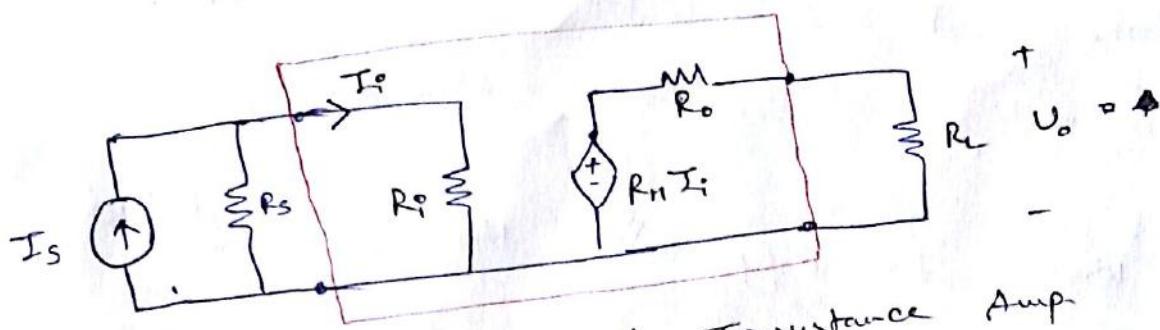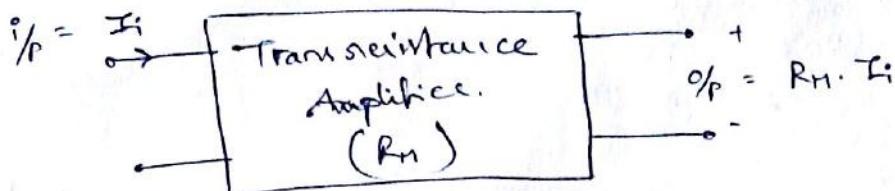A. Transresistance Amplifier: ($R_m = \frac{U_o}{I_i}$)

This accepts current as input signal and produces voltage as output signal.



F'ns: Equivalent circuit of Transresistance Amp.

$$I_o = I_i = \frac{R_s}{R_s + R_i} \cdot I_s \quad \text{and} \quad U_o = \frac{R_L}{R_L + R_i} \cdot R_m \cdot I_i$$

if $R_i \ll R_s$ and $R_o \ll R_L$ then $U_o \approx R_m \cdot I_s$

* Characteristics of Transresistance Amp:

1. Very high & stable transresistance gain (R_m)

2. Very high BW

3. very low $R_i \ll R_o$.

* Ideal characteristics of Transresistance Amp:

1. $R_m = \infty$

3. $BW = \infty$

2. Stable R_m

4. $R_i = 0$ and $R_o = 0$

* Ideal Transresistance Amp has ~~negative~~ zero input impedance and ~~infinity~~ zero output impedance.

Disadvantages of Basic Amplifiers.

1. The instability of a.c. gain is due to
 - (a) change in power supply (ie drift in Supply)
 - (b) changes in h-parameters
 - (c) Aging of the device
2. The input and output impedances are not according to the requirements.
3. Large ~~high~~ frequency and Harmonic distortions.
4. Noise is large.
5. Bandwidth is not sufficient

Remedy: By using feedback, we can improve the performance

of Basic amplifiers

Feedback: It is a process of application of a part of the o/p giving back to the input.

Feedback is of two types : $+ve_{FB}$ and $-ve_{FB}$.

* If the feedback signal gets added to the applied if signal, such that the magnitude of effective input signal to the amp increases, then it is called $+ve_{FB}$. $+ve_{FB}$ in a controlled form is applied, amplifier behaves as oscillator.

* If the feedback signal gets ~~added~~ subtracted from the applied input signal, such that the magnitude of effective input signal to the amplifier reduces - then it is called as $-ve\text{FB}$.

$-ve\text{FB}$ is used in amplifiers, to overcome the disadvantages of basic amplifier.

Differences between $+ve\text{FB}$ and $-ve\text{FB}$


$+ve\text{FB}$

1. Def
2. effective input to basic amp ~~reduces~~ increases.
3. gain \uparrow
4. BW \downarrow
5. Input and output impedances degraded
6. Noise & distortion \uparrow
7. Stability in gain \downarrow
8. feedback network is frequency sensitive
9. β_{new} consists of L or C ~~and~~ or both Components
10. +ve FB is useful only when it is applied in a controlled manner i.e. $A_f\beta = 1$
ie $|A_f\beta| = 1$ and $|A_f\beta| = 1$.
11. oscillator uses.

$-ve\text{FB}$

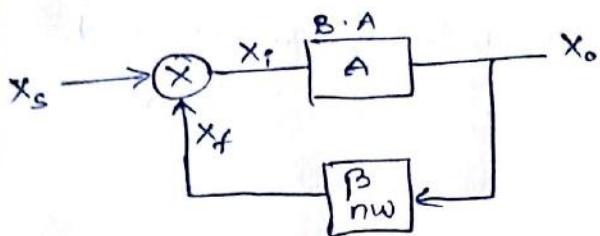1. Def
2. effective input to Basic amp ~~reduces~~ Reduces
3. Gain \downarrow
4. BW \uparrow
5. Input and output impedances improves.
6. Noise & distortion \downarrow
7. stability in gain \uparrow
8. feedback nw. (β_{new}) is independent of frequency.
9. β_{new} consists of only resistor.
10. No condition exists for $-ve\text{fb}$
ie. any amount of o/p can be fed back to output.
11. Amplifiers use $-ve\text{FB}$.

General Block diagram of Feedback Amplifiers:



$A = \text{gain of Basic Amplifier}$
 $\text{gain of Amp w/o Feedback.}$

$$A = \frac{X_o}{X_i} = \text{open loop gain}$$

$$A_f = \text{gain of amp with FB} = \text{Closed loop gain} = A_f = \frac{X_o}{X_s}$$

$$\begin{aligned} \beta &= \text{gain of Feedback network} \Leftrightarrow \text{feedback factor} \\ &= \text{reverse transmission factor} = \frac{X_f}{X_o} \end{aligned}$$

X_s = applied input signal

$$X_f = \text{feed back signal} = \beta X_o$$

$$X_i = \text{effective input signal} = X_s \pm X_f$$

if $X_i = X_s + X_f$ then positive FB.

if $X_i = X_s - X_f$ then Negative FB

(a) for +ve FB: (Derivation of closed loop gain)

we know for +ve FB, $X_i = X_s + X_f = X_s + \beta X_o$

$$X_i = X_s + \beta(A X_i) = X_s + A\beta X_i$$

$$X_i(1 - A\beta) = X_s$$

$$\text{closed loop gain} = A_f = \frac{X_o}{X_s} = \frac{X_o}{X_i(1 - A\beta)} = \frac{A}{1 - A\beta}$$

for -ve FB, $A_f > A$ i.e. gain increases.

(b) closed loop gain for -ve FB:

$$\text{for -ve FB, } X_i = X_s - X_f = X_s - \beta X_o = X_s - \beta(A X_i) = X_s - A\beta X_i$$

$$X_i(1 + A\beta) = X_s \therefore \text{closed loop gain} = A_f = \frac{X_o}{X_s} = \frac{X_o}{X_i(1 + A\beta)}$$

$$A_f = \frac{A}{1 + A\beta} \therefore A_f < A \text{ i.e. gain reduced when -ve FB is used.}$$

Effects of -ve FB (Adv. of -ve FB)

(1) effect of -ve FB on Gain stability

$$\text{closed loop gain} = A_f = \frac{A}{1+AB} \approx \frac{A}{AB} = \frac{1}{B}$$

closed loop gain depends only on B now, since B now is resistive, which is independent of h-parameter. Hence closed loop gain is more simple and easier. Hence closed loop gain is more stable.

Another view:

Differentiate w.r.t. A

$$A_f = \frac{A}{1+AB} \Rightarrow \frac{dA_f}{dA} = \frac{(1+AB)(1) - (A)(B)}{(1+AB)^2} = \frac{1}{(1+AB)^2}$$

$$\frac{dA_f}{dA} = \frac{1}{(1+AB)^2}$$

Multiply & Divide with A :

$$\frac{dA_f}{dA} = \frac{A}{A} \cdot \frac{1}{(1+AB)} \cdot \frac{1}{(1+AB)} = \frac{A_f}{A} \left(\frac{1}{1+AB} \right)$$

So arrange the equation:

$$\boxed{\frac{dA_f}{A_f} = \frac{1}{1+AB} \cdot \frac{dA}{A}}$$

where $\frac{dA_f}{A_f} = \text{relative change in gain with FB}$

$\frac{dA}{A} = \text{(fractional change) in gain without FB.}$

* for -ve FB, $\left| \frac{dA_f}{A_f} \right| \ll \left| \frac{dA}{A} \right|$

(2) Sensitivity factor of FB (S): is defined as

$$S = \frac{(dA_f/A_f)}{(dA/A)} = \frac{1}{1+A_f}$$

Desensitivity factor (D) is reciprocal of Sensitivity.

$$D = \frac{1}{S} = 1 + A_f$$



Ideal value of Desensitivity factor = ∞

Ideal value of Sensitivity factor = 0

Ideal value of

- * Desensitivity (D) Measures the stability of $-veFB$ i.e. how much the gain is desensitive (stable) w.r.t. temperature, aging and frequency.
- Higer the value of D , More stability.

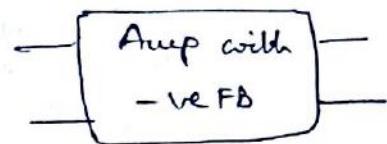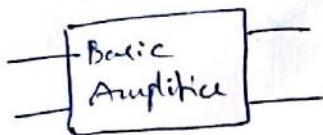Effect of -ve FB on Bandwidth (i.e. on f_L and f_H).



Let $A = \text{Gain of B.A. at MF}$

$A_L = \text{Gain of B.A. at LF}$

$A_H = \text{Gain of B.A. at HF}$

$f_L = \text{lower Cutoff frequency of B.A.}$

$f_H = \text{Upper Cutoff frequency of B.A.}$

We know Amplifier behaves as
HP RC ckt (HPF) at Low freq.

and as LPF at High freq.

So, the value of A_L and A_H

can be expressed as

$$A_L^{(f)} = \frac{A}{1 - j(f/f_L)} \quad \text{and}$$

$$A_H^{(f)} = \frac{A}{1 + j(f/f_H)}$$

Let $A_f = \text{Gain of Amp with FB at MF}$

$A_{Lf} = \text{Gain of Amp with FB at LF}$

$A_{Hf} = \text{Gain of Amp with FB at HF}$

$f_{Lf} = \text{lower Cutoff freq. of amp with FB}$

$f_{Hf} = \text{upper Cutoff freq. of amp with FB}$

We know Gain of amplifier reduces
 $\frac{A_f}{(1+A_f)/\beta}$ when -ve FB is used.

So

$$\text{at MF}, \quad A_f = \frac{A}{1 + A_f \beta}$$

$$\text{at LF}, \quad A_{Lf}^{(f)} = \frac{A_L}{1 + A_L \beta}$$

at HF,

$$A_{Hf}^{(f)} = \frac{A_H}{1 + A_H \beta}$$

(a) effect of -ve FB on lower cutoff frequency:

We know, the gain of an amplifier with FB at LF is

$$A_{Lf}^{(f)} = \frac{A_L(f)}{1 + A_L(f)\beta} = \cancel{\frac{A_L(f)}{1 + A_L(f)\beta}}$$

$$= \frac{\frac{A}{1 - j(f/f_L)}}{1 + \frac{A}{1 - j(f/f_L)} \beta} = \frac{A}{1 + A\beta - j f_L / f} = \frac{(A/1 + A\beta)}{1 - j \frac{f_L}{f(1 + A\beta)}} = \frac{A_f}{1 - j \frac{f_L}{f}}$$

where f_{L_f} = lower cutoff frequency of amp with FB = $f_L / (1 + AB)$

$$f_{L_f} = \frac{f_L}{1 + AB} \quad \text{so } f_{L_f} < f_L$$

i.e. -ve FB reduces the the Magnitude of lower cutoff freq by $(1+AB)$ times when Compared to Basic Amplifier

(b) Effect of -ve FB on Upper Cutoff frequency:

we know the gain of an amp with FB ~~with~~ at HF is

$$A_{H_f}(+) = \frac{A_H(f)}{1 + A_H(f)B} = \frac{\left(\frac{A}{1 + j f/f_H}\right)}{1 + \frac{A}{1 + j f/f_H} \cdot B}$$

$$A_{H_f}(f) = \frac{A}{(1 + AB + j(f/f_H))} = \frac{(A/1 + AB)}{1 + j \frac{f}{f_H(1 + AB)}} = \frac{Af}{1 + j f/f_{H_f}}$$

where f_{H_f} = Upper cutoff frequency of amp with FB

$$f_{H_f} = f_H(1 + AB) \quad \text{so } f_{H_f} > f_H.$$

i.e. -ve FB increases the Magnitude of Upper cutoff frequency by $(1+AB)$ times Compared to Basic Amp.

(c) effect of -ve FB on Bandwidth:

Def: Bandwidth is a range of frequencies over which the gain is greater than or equal to 70.7% of its Maximum value

Gain falls to 70.7% of its Max. value at ~~at~~ $\frac{1}{\sqrt{2}}$.
Upper and lower Cutoff frequencies. (or) the frequency
at which gain reduces to 70.7% ($\frac{1}{\sqrt{2}}$) of its Max. value
is called Cutoff frequency.


Bandwidth of Basic Amp = $f_H - f_L$

Since $f_H \gg f_L$, so BW of B.A $\approx f_H$.

Bandwidth of Amp with FB = $f_{H_f} - f_{L_f}$

$$\begin{aligned}\text{Since } f_{H_f} \gg f_{L_f}, \text{ so } (\text{BW})_f &= f_{H_f} \cdot = f_H(1+AP) \\ &= \text{BW}(1+AP)\end{aligned}$$

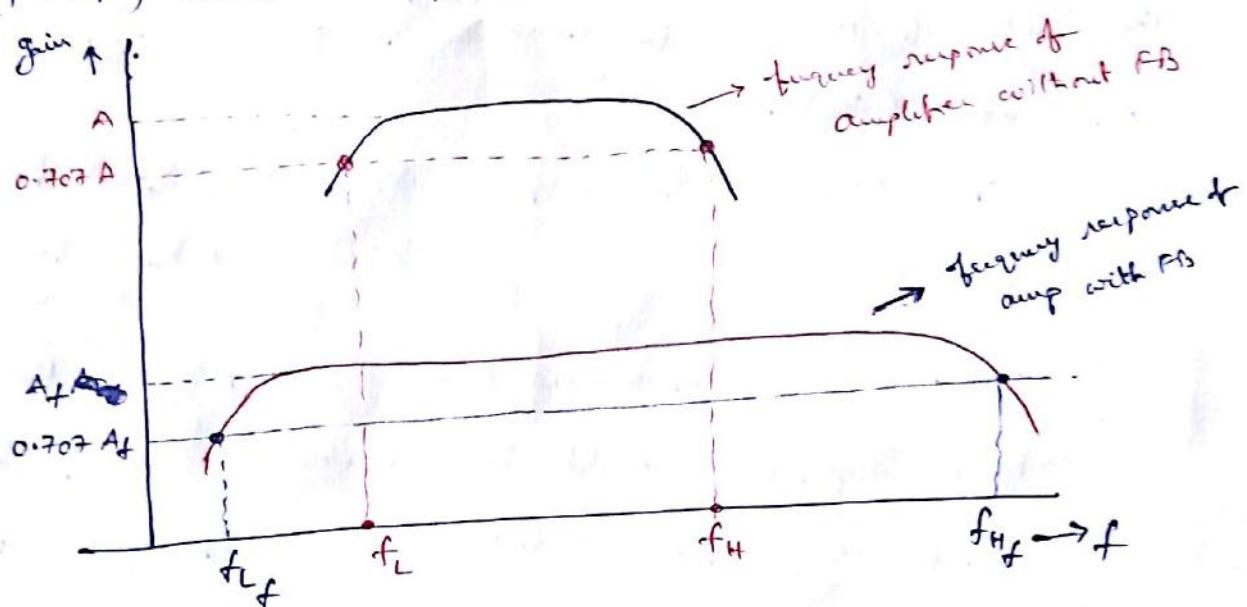Hence BW of an amplifier increases with $-ve\text{FB}$ by $(1+AP)$ times compared to Basic amplifier.



* Try using FB, Gain Bandwidth product of Amplifier doesn't change i.e. it remains constant

Proof Gain BW product of B.A = $(A) (\text{BW})$


$$\text{Gain BW product of Amp with FB} = A_f \cdot (\text{BW})_f$$

$$= \left(\frac{A}{1+AP}\right) ((\text{BW})(1+AP)) = (A)(\text{BW}).$$

$$\therefore A_f \cdot (\text{BW})_f = A \cdot (\text{BW})$$

Types of Feedback Topologies

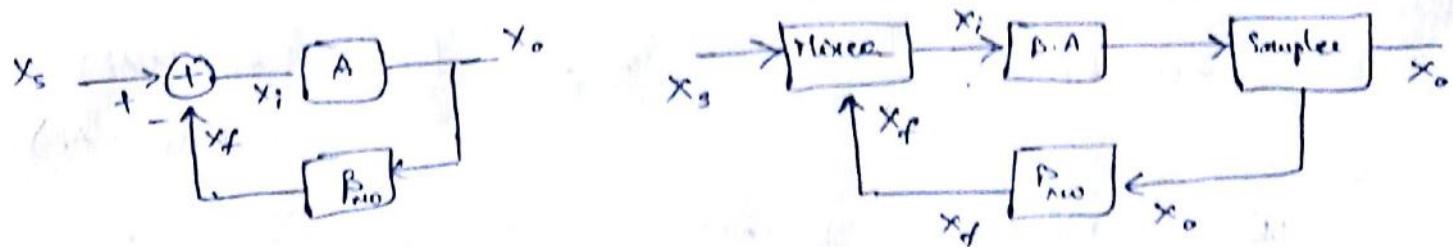The general block diagram of -veFB amplifier is



The function of mixer is to ^{Add/subtract} ~~Combine~~ feedback signal with applied input signal (x_s).

$$\% \text{ of } \beta_{\text{FWB}} = \text{effective i/p} = x_i = x_s - x_f \quad \text{for -veFB}$$

$$x_i = x_s + x_f \quad \text{for +veFB}$$

The function of sampler is that it will provide ^{the entire} ~~the~~ % of basic amplifier should be available at the i/p of β_{FWB} , such that β_{FWB} selects how much part of o/p should be given as feedback (~~$x_f = \%$~~ $x_f = \% \text{ of } \beta_{\text{FWB}} = \beta x_o$).

Feedback topology is a method of providing feedback based on how the o/p signal is sampled and how the feedback signal is combined at i/p of amp.

There are four different feedback topologies.

- | | | |
|---------------------|------|-----------------|
| 1) Voltage - Series | (or) | Series - Shunt |
| 2) Voltage - Shunt | (or) | Shunt - Shunt |
| 3) Current - Series | (or) | Series - Series |
| 4) Current - Shunt | (or) | Shunt - Series |

Feedback Topologies

Based on Mixing law



If X_s , X_f and X_i are

Voltage Signals




They must be combined in series, so that

$$V_i = V_s - V_f.$$



Series Mixing

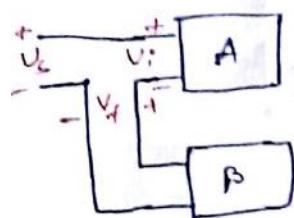

Current Signals




They must be combined in shunt.

$$\text{so } I_i = I_s - I_f$$



Shunt Mixing

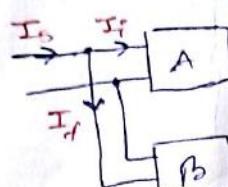

Based on Sampling law



If X_o is


Voltage



If must be given in parallel to the power input.



Shunt Sampling or
Voltage Sampling

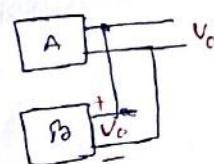


Current



If must be given in series to the power input.




Power Sampling or

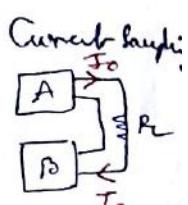

Identification of Mixing Methods:

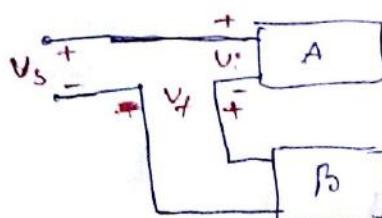
(a) If the feedback signal is in series with the external i/p signal, then it is series mixing.

In series mixing, X_s , X_f and X_i are all voltage signals, because currents can't be mixed up in series.



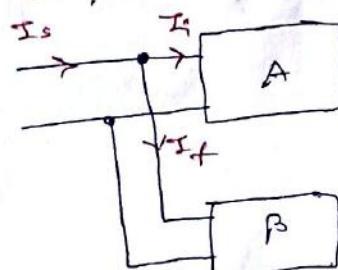
(b) If the feedback signal is in parallel with the external i/p signal, then it is shunt mixing.

In shunt mixing, X_s , X_f and X_i are all current signals, because voltages can't be mixed up in parallel.




Identification of Sampling network

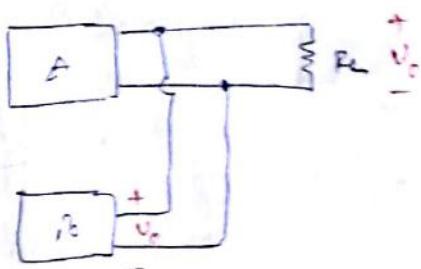(a) If the sampled signal is taken at the o/p node itself, then it is a voltage sample i.e. if the load and the p/n are connected to the same node, then op sampling is short.



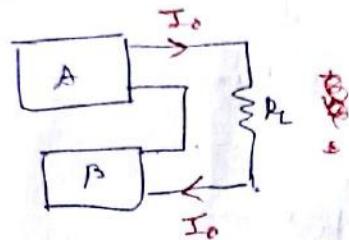(b) If the sampled signal is taken from the o/p loop, then it is a current sample i.e. if one terminal of the output active device is driving the load and the other terminal is attached to the feedback network then the output sampler is series.




Comprehension of Different Topologies:

1. X_f, X_s, X_i	Voltage	Voltage	Current	Current
2. Type of Mixing	Series Mixing	Series Mixing	Shunt Mixing	Shunt Mixing
3. X_o	Voltage	Current	Voltage	Current
4. Type of Sampling	Shunt Sampling	Series Sampling	Shunt Sampling	Series Sampling
5. feed topology				
(a) output - input	Voltage - Series	Current - Series	Voltage - Shunt	Current - Shunt
(b) input - output	Series - Shunt	Series - Series	Shunt - Shunt	Shunt - Series
6. Basic Amp. Type ($\frac{X_o}{X_i}$)	Voltage amp (A_v)	Transconductance Amp (G_m)	Transresistance Amp (R_{in})	Current Amp (A_I)
7. Ideal value of				
(a) input impedances (R_{iideal}, R_{fideal})	∞	∞	0	0
(b) output impedance (R_{oideal})	0	∞	0	∞
8.(a) R_{if}	$R_i(1+A_{IB})$	$R_i(1+G_m\beta)$	$R_i/(1+R_{IF}\beta)$	$R_i/(1+A_{IB}\beta)$
(b) R_{of}	$R_o(1+A_{IB})$	$R_o(1+G_m\beta)$	$R_o/(1+R_{IF}\beta)$	$R_o(1+A_{IB}\beta)$
9. Drawing Basic Amp				
(a) To find input put loop. set	$V_o = 0$	$I_o = 0$	$V_o = 0$	$I_o = 0$
(b) To find % loop. set	$I_i = 0$	$I_i = 0$	$V_i = 0$	$V_i = 0$
10. practical feedback class	CC amp, CD amp, (current follower, source follower)	CE amp, CS amp,	Feedback with FB resistor from C(D) to B(A),	Cascade of Two CE stages with FB from 2nd emitter to first base through resistor, R' .

Effect of -ve FB on Input and Output resistances.

(1) Voltage - Series Feedback:

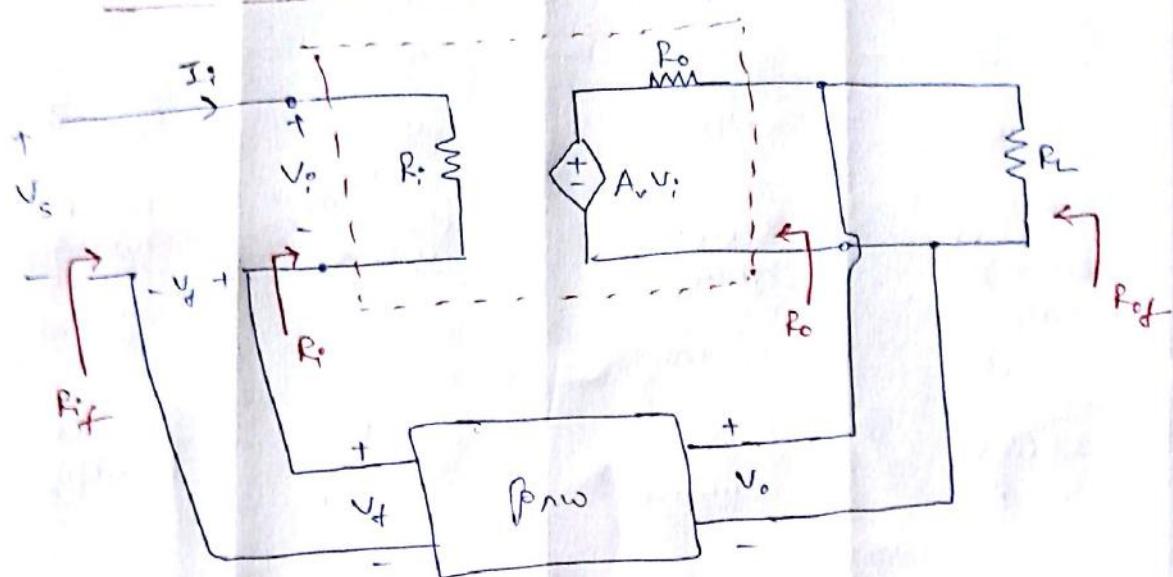

(a) Since the feedback signal V_f opposes V_s , the input current

I_i is less than it would be if V_f were absent. Hence

the i/p resistance with feedback, $R_{if} \approx \frac{V_s}{I_i}$ is greater than

the i/p resistance without feedback, $R_i \cdot (= \frac{V_i}{I_i})$

Let A_v = open circuit voltage gain (taking R_s into account).

$$R_{if} = \frac{V_s}{I_i} = \frac{V_i + V_f}{I_i} = \frac{I_i R_i + \beta V_o}{I_i} = \frac{I_i R_i + \beta (A_v \cdot V_i)}{I_i}$$

$$R_{if} = \frac{\cancel{I_i R_i} + \beta (A_v \cdot I_i R_i)}{I_i} = I_i \frac{(R_i + A_v \beta R_i)}{I_i}$$

$$R_{if} = R_i + A_v \beta R_i = R_i (1 + A_v \beta)$$

Hence i/p resistance with series mixing is increased.

(b) Effect of FB on O/P resistance:

* Negative Feedback which samples the O/p voltage, regardless of how this O/p signal is returned to the input, tends to decrease the O/p resistance.

Let R_{of} = output resistance with FB, looking into the O/p terminals but with R_L disconnected.

To find R_{of} ,



(i) we must remove externally applied i/p signal ie.

~~we set~~ $V_s = 0$.

(ii) Remove R_L (ie. $R_L = \infty$).

(iii) Apply a voltage V across the O/p terminals, and calculate the current I delivered by V .

$$\text{Then } R_{of} = \frac{V}{I}$$

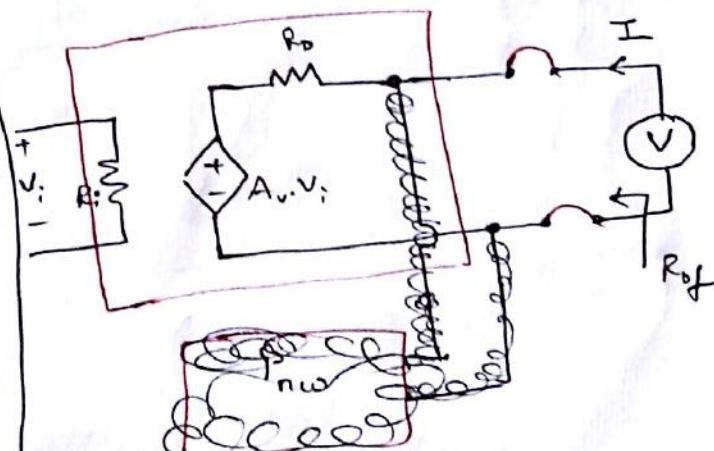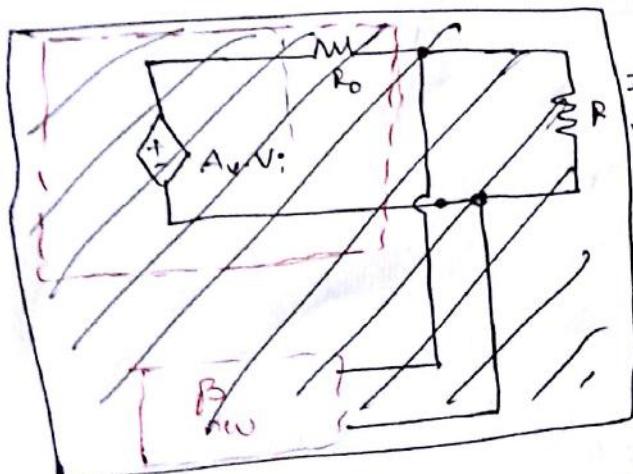

$$I = \frac{V - A_v V_i}{R_o} = \frac{V - A_v (V_s - V_f)}{R_o}$$

$$\text{Since } V_s = 0, \quad I = \frac{V - A_v V_f}{R_o} = \frac{V - A_v (FV)}{R_o} = \frac{V (1 + A_v \beta)}{R_o}$$


$$\text{Hence } R_{of} = \frac{V}{I} = \frac{R_o}{1 + A_{uf}B}$$

and R'_{of} = output resistance with FB added
including R_L

$$R'_{of} = R_{of} \parallel R_L$$

In other way $R'_{of} = \frac{R_o}{1 + A_{uf}B}$ column $R'_{of} = R_o \parallel R_L$

(2) Current - Shunt Feedback:

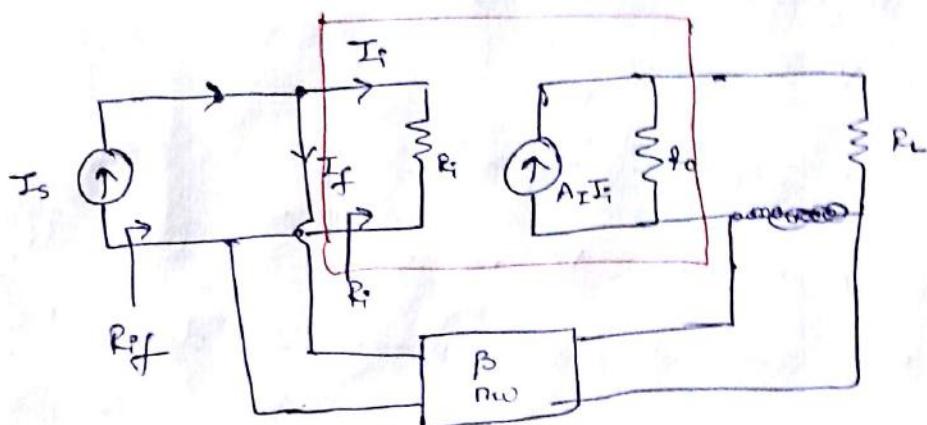

(a) $R_{if} = \text{input impedance with FB} = \frac{V_i}{I_s}$
 $R_{if} = \text{input impedance with FB} = \frac{V_i}{I_i}$

$$R_i = \text{input impedance of B.A} = \frac{V_i}{I_i}$$


$$I_s = I_i + I_f = I_i + A_2 I_o = I_i + A_2 B I_i$$

$$I_s = I_i (1 + A_2 B)$$

$$\therefore R_{if} = \frac{V_i}{I_s} = \frac{V_i}{I_i (1 + A_2 B)} = \frac{R_i}{1 + A_2 B}$$

Hence shunt mixing reduces the $\%P$ resistance of B.A by $(1 + A_2 B)$ times.

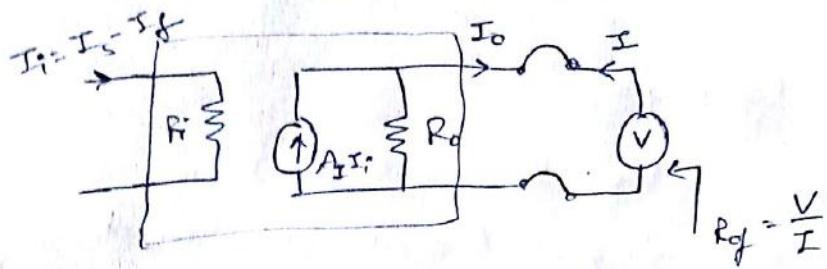(iii) effect of -ve F/B on o/p impedance:



from KCL at output node, $I + A_I I_i - \frac{V}{R_o} = 0$

$$I = \frac{V}{R_o} - A_I I_i = \frac{V}{R_o} - A_I (I_s - I_f)$$

Since $I_s = 0$, while calculating o/p impedance,

$$I = \frac{V}{R_o} - A_I (-I_f) = \frac{V}{R_o} + A_I (\beta I_o)$$

$$\text{but } I_o = -I, \text{ so } I = \frac{V}{R_o} - A_I \beta I$$

$$I + A_I \beta I = \frac{V}{R_o}$$

$$I (1 + A_I \beta) = \frac{V}{R_o}$$

$$\therefore R_{of} = \frac{V}{I} = R_o (1 + A_I \beta).$$

Hence o/p impedance of basic amplifier with shunt
Sampling increases by a factor of $(1 + A_I \beta)$.

ANALYSIS OF A FEEDBACK AMPLIFIER:

Procedure:


1. Identify the topology
2. Draw the basic amplifier circuit without FB, but by taking the loading of the source into account, which is obtained by applying following rules.
 - (a) To find the input circuit:
 - (i) Set $V_o = 0$ for voltage sampling i.e. short the op node.
 - (ii) Set $I_o = 0$ (open the op loop) for current sampling
 - (b) To find the Output circuit:
 - (i) Set $V_i = 0$ (short the i/p node) for shunt mixing
 - (ii) Set $I_i = 0$ (open the i/p loop) for series mixing.
3. Replace each active device by the proper model i.e. the hybrid- π model for a Tr. at HF and h-parameter (or) r -parameter (or) Hybrid or LF model at low frequencies
4. Indicate X_f and X_o then calculate $\beta = \frac{X_f}{X_o}$
5. Evaluate 'A' by using KCL or KVL to the equivalent circuit
6. From A and β values,
find $D = 1 + AB$
 $A_f = A / 1 + AB$
 $R_{if} =$
 $R_{of} =$

VOLTAGE - SERIES FB:

e.g.

emitter follower, source follower

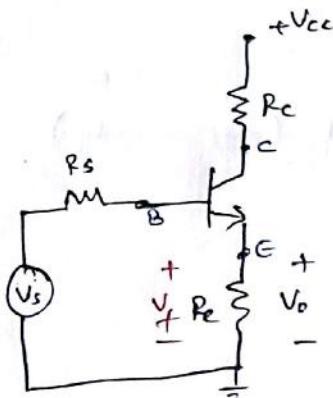(1) EMITTER FOLLOWER C Common Collector Amplifier:



S1: For the given ckt,

the feedback signal V_F is the voltage across R_F (V_F), which is in series with oppt input signal, V_s .

So Series Mixing.

Since the o/p and feed back are taken at same node, the output Sampling is shunt (or voltage Sampling).


Hence the topology involved is

Voltage-Series (or)


Series-Shunt.

S2: Draw the Basic Amplifier ckt without FB, but taking the loading of β now into account
(a) To find input ckt, set $V_o = 0$ for voltage sampling.

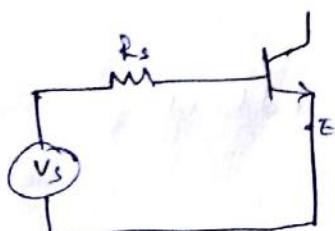then R_E will not appear in the input loop, hence V_s in series with R_S , appears between B and E.




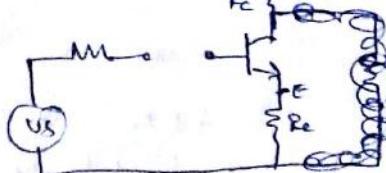(b) To find the output ckt, set $I_B = 0$ for Series Mixing.
i.e. Open the input loop formed by the voltages - i.e. $I_B = 0$



Now R_E appears in o/p side only, as there is no ip Current ($I_B = I_E = 0$) is flowing

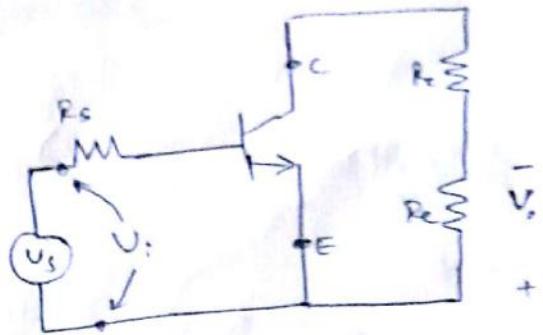
Now the ~~actual~~ ckt represents its equivalent



Assume R_s is part of amp.

$$\therefore V_i = V_s$$

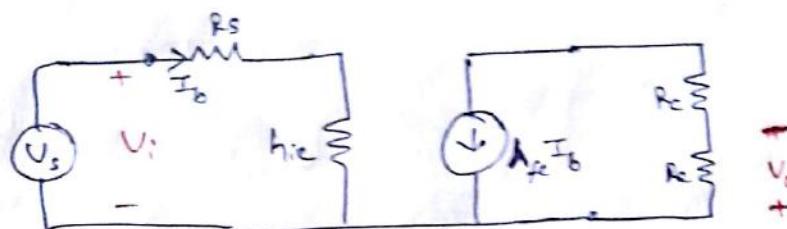S₃: Replace BJT with h-parameter model. (approximate).



$$A_v = \frac{V_o}{V_i} = \frac{h_{fe} I_b R_c}{V_s} = \frac{h_{fe} I_b R_c}{I_b (R_s + h_{ie})} = \frac{h_{fe} R_c}{R_s + h_{ie}}$$

$$\beta = \frac{X_f}{X_i} = \frac{V_f}{V_i} = 1$$

$$D = 1 + A_v \beta = 1 + \frac{h_{fe} R_c}{R_s + h_{ie}} = \frac{R_s + h_{ie} + h_{fe} R_c}{R_s + h_{ie}}$$

$$A_{vf} = \frac{A_v}{D} = \frac{A_v}{1 + A_v \beta} = \frac{h_{fe} \cdot R_c}{R_s + h_{ie}} \times \frac{R_s + h_{ie}}{R_s + h_{ie} + h_{fe} R_c}$$

$$A_{vf} = \frac{h_{fe} \cdot R_c}{R_s + h_{ie} + h_{fe} \cdot R_c} \approx 1. \text{ i.e. emitter follower}$$

R_i = input impedance without feedback (i.e. from the coupling cat)

$$R_i = R_s + h_{ie}$$

$$R_{if} = R_i (1 + A_v \beta) = (R_s + h_{ie}) \left(\frac{R_s + h_{ie} + h_{fe} R_c}{R_s + h_{ie}} \right)$$

$$R_{if} = R_s + h_{ie} + h_{fe} \cdot R_c$$

Since we used simplified h-parameter, $h_{oc} = 0$ i.e. $R_o = \infty$


$$\therefore R'_o = R_c // R_o = R_c \quad \therefore R'_o = \frac{R_o}{1 + A_v \beta} = \frac{R_c (R_s + h_{ie})}{R_s + h_{ie} + h_{fe} \cdot R_c}$$

- * The voltage series FB deenergizes voltage gain w.r.t. changes in load and also increases the input resistance, and decreases the o/p resistance.

Fundamental Assumptions for feedback Amp Analysis:

1. The input signal is transmitted to the o/p through the amplifier 'A' but not through the β network.
i.e. if the Amplifier (A) is deactivated,
(say, set $A=0$ by reducing $\beta \cdot h_{fe}=0$ for BJT, $g_m=0$ for FET)
then the output signal must drop to zero.
2. The feedback signal is transmitted from the o/p to the i/p through β netw., but not through the amplifier.
i.e. the basic amplifier is Unilateral from input to output, and the reverse transmission is zero.
3. The reverse transmission factor, β of the ~~network~~
feedback network is independent of the load and
the source resistances (R_L and R_S).

(b) FET Source Follower:

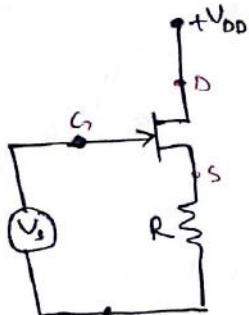

S: Identify the topology.

Since the feedback signal, V_f is the voltage across ' R ', which is in series with applied i/p voltage, V_s , so Series Tapping.

Since the o/p and β netw. are at the same node it is Voltage Sample or Shunt Sample.

Hence the topology is "Voltage-series" or "Series - shunt".

Q. To draw basic amplifier with loading of pmos,

w To find the input ckt, set $V_o = 0$ (short the o/p node).

Hence $V_s = V_i$ i.e. V_s appears directly between Gate and Source





ch

To find the o/p ckt, set $I_d = 0 \Rightarrow R_{ds} \rightarrow \infty$ i.e. break the input loop formed at input side now R appears only in the output loop.

Now draw the equivalent ckt.

S₃: Replace FET with equivalent model.

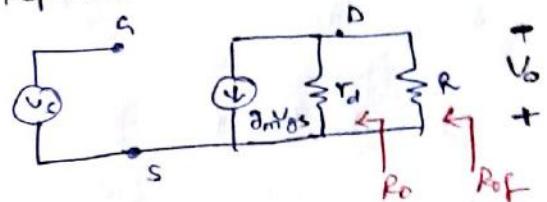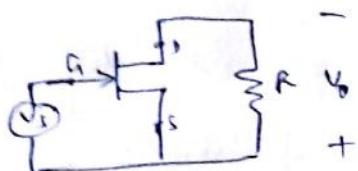

S₄: Calculate A_v , β , A_{vf} , R_{if} , R_{of} .

$$A_v = \frac{V_o}{V_s} = \frac{g_m V_{gs} (\gamma_d // R)}{V_{gs}} = g_m (\gamma_d // R) = \frac{g_m \gamma_d R}{\gamma_d + R} = \frac{m \cdot R}{\gamma_d + R}$$

$$\beta = \frac{V_f}{V_o} = 1.$$

$$1 + A_v \beta = 1 + \frac{m \cdot R}{\gamma_d + R} = \frac{\gamma_d + R + m \cdot R}{\gamma_d + R} = \frac{\gamma_d + (1+m)R}{\gamma_d + R}$$

$$A_{vf} = \frac{A_v}{1 + A_v \beta} = \frac{m \cdot R}{\gamma_d + R(1+m)} \approx 1.$$

Since R_o of FET is very large bcz RB is junction,

$$R_{if} = R_o (1 + A_v \beta) = \infty$$


$$R_o = \gamma_d \text{ and } R_{of} = R // \gamma_d$$

$$R_{of}' = \frac{R_{of}}{1 + A_v \beta} = \frac{(R // \gamma_d)}{1 + \frac{m \cdot R}{\gamma_d + R}} = \frac{R \cdot \gamma_d}{\gamma_d + R(1+m)}$$

Hence Voltage - series FB deenergizes Voltage gain and increases its resistance and decreases the o/p resistance

2. CURRENT-SERIES Feedback

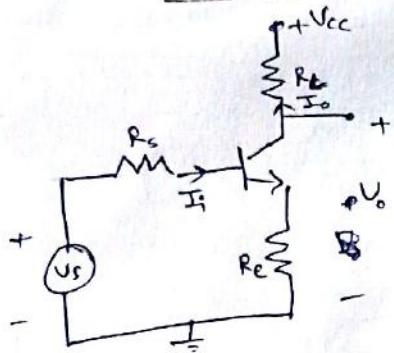(a) CE amplifier with emitter resistor, R_E (CE with R_E)



S₁: The feedback signal is the voltage, V_f , across R_E , which is in series with the applied input signal, V_S .

Hence Series Mixing.

$$V_O = V_{CE} + I_E R_E = V_{CE} + V_f$$

Since the feedback signal is a part of output loop, the type of sampling is Current Sample.



The topology is Current-Seried (or) Series-Series feedback.

S₂: Draw Basic amp by Considering the loading of B_{NW} .

(a) To draw i/p side, set $I_o = 0$ for Current Sampling. So no o/p current flows in the R_E , the current that flows in R_E is the input current i.e. I_i or I_b .


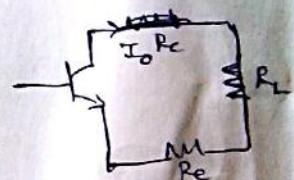
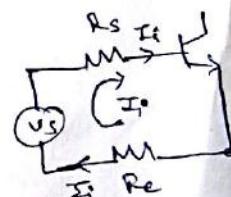
(b) To draw o/p side, set $I_i = 0$ i.e.



break the loop at input for series mixing
So only output current flows in R_E i.e. R_E should present in only outside.



Combine both circ. to get Basic amp with loading of B_{NW} .

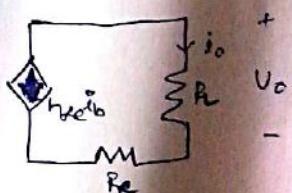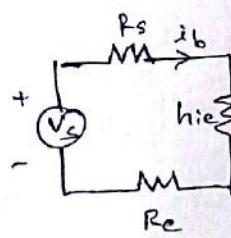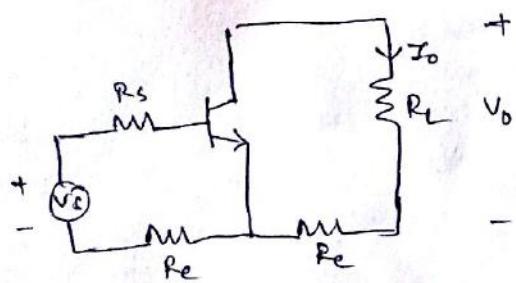S₃: replace Tr symbol with approximate h-parameter model.



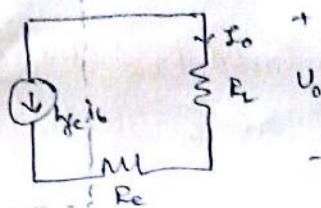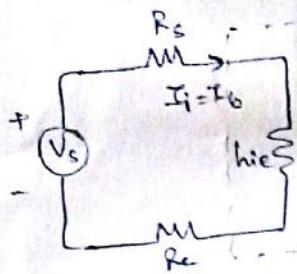

$$\text{S.A. } A = \text{gain} \quad B \cdot A = \frac{V_o}{V_i}$$

$$A = \frac{I_o R_L}{I_e h_{ie}} = -\frac{h_{fe} I_o R_L}{h_{ie}}$$

$$A = -\frac{h_{fe} R_L}{h_{ie}}$$

$$\beta = -\frac{X_f}{X_o} = \frac{V_f}{I_o} = -\frac{I_o R_L}{I_o} = -R_L$$

V* If we think, ~~that V_o is the output~~,
 I_o is proportional to V_o , it is not correct to conclude that this
is a voltage-series feedback. Thus, if the o/p signal is
taken as the Voltage V_o , then $\beta = \frac{V_f}{V_o} = -\frac{I_o R_L}{I_o R_L} = -R_L$

Since β is now a function of the load R_L , but the
assumption of β now should be independent of R_L and R_s is
going wrong.

Current series FB has basic amplifier is Transconductance amp,

$$\text{cathode gain in } G_m = \frac{X_o}{X_i} = \frac{I_o}{V_i} = -\frac{h_{fe} i_b}{i_b (R_s + h_{ie} + R_L)}$$

$$G_m = \frac{-h_{fe}}{R_s + h_{ie} + R_L} \quad \text{and} \quad \beta = -R_L$$

$$D = \text{Decoupling factor} = 1 + G_m \cdot \beta = 1 + \frac{h_{fe} R_L}{R_s + h_{ie} + R_L}$$

$$D = \frac{R_s + h_{ie} + R_L (1 + h_{fe})}{R_s + h_{ie} + R_L}$$

$$G_{mF} = \text{gain of transconductance with FB} = \frac{G_m}{D} = \frac{G_m}{1 + G_m \beta}$$

$$G_{mF} = \frac{-h_{fe}}{R_s + h_{ie} + R_L (1 + h_{fe})} = \frac{X_o}{X_s} = \frac{I_o}{V_s}$$

$$\therefore I_o = G_{mF} \cdot V_s = \frac{-h_{fe} \cdot V_s}{R_s + h_{ie} + R_L (1 + h_{fe})}$$

$$\text{Since } R_L (1 + h_{fe}) \gg R_s + h_{ie} \text{ and } h_{fe} \gg 1, \quad I_o = -\frac{V_s}{R_L}$$